

# COMPUTER SCIENCE & IT

## DIGITAL LOGIC



Lecture No: 04

Sequential Circuit



By- Chandan Gupta Sir

# Recap of Previous Lecture




- Race Around condition
- Counter
-






# Topics to be Covered

Counter

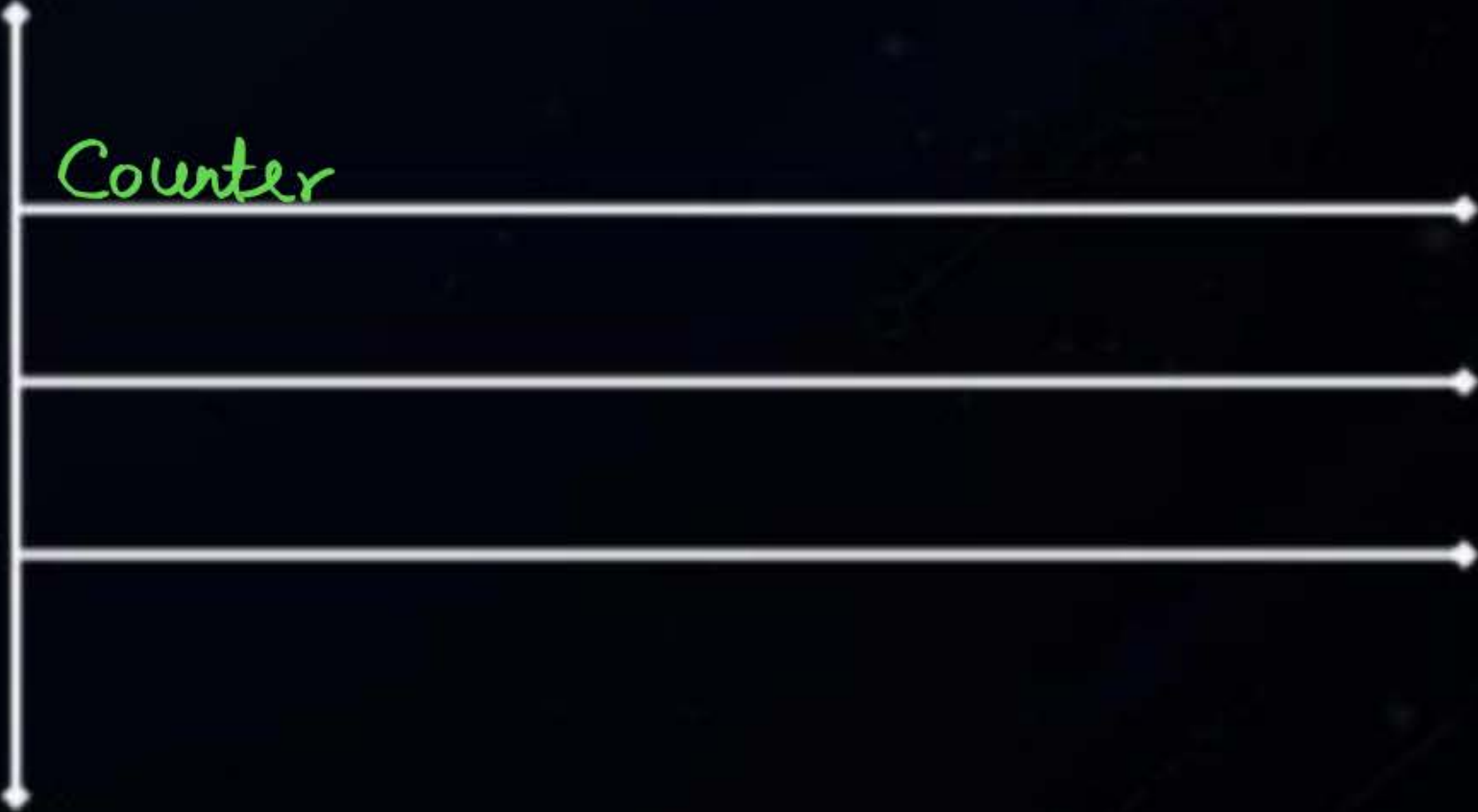

• 0-0-1-1-2-2-2-3-3-3-3 → MOD no. = 11

• 0-1-3-2 → MOD no. = 4 → 2ff

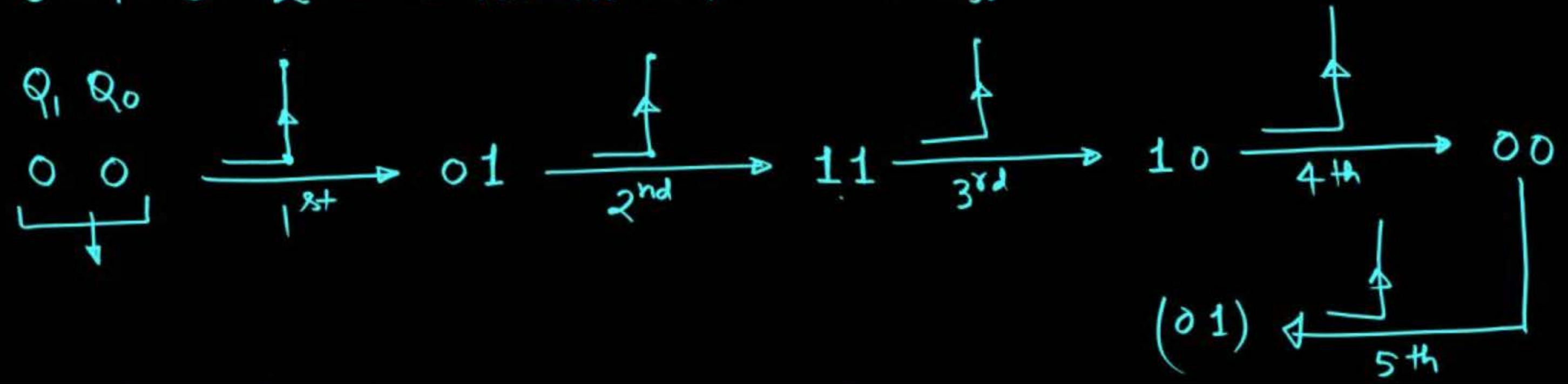


- Note: After application of MOD no. of clock pulses counter will again be at the starting state.
- After application of integer multiple of MOD no. of clock pulses counter will again be at starting state.



if starting state is  $(3)_{10}$  then after 263 clock pulses, what will be the state of the counter  $(1)_{10}$

$$(3)_{10} \xrightarrow{4\text{CLK}} (3)_{10} \xrightarrow{4\text{CLK}} (3)_{10}$$
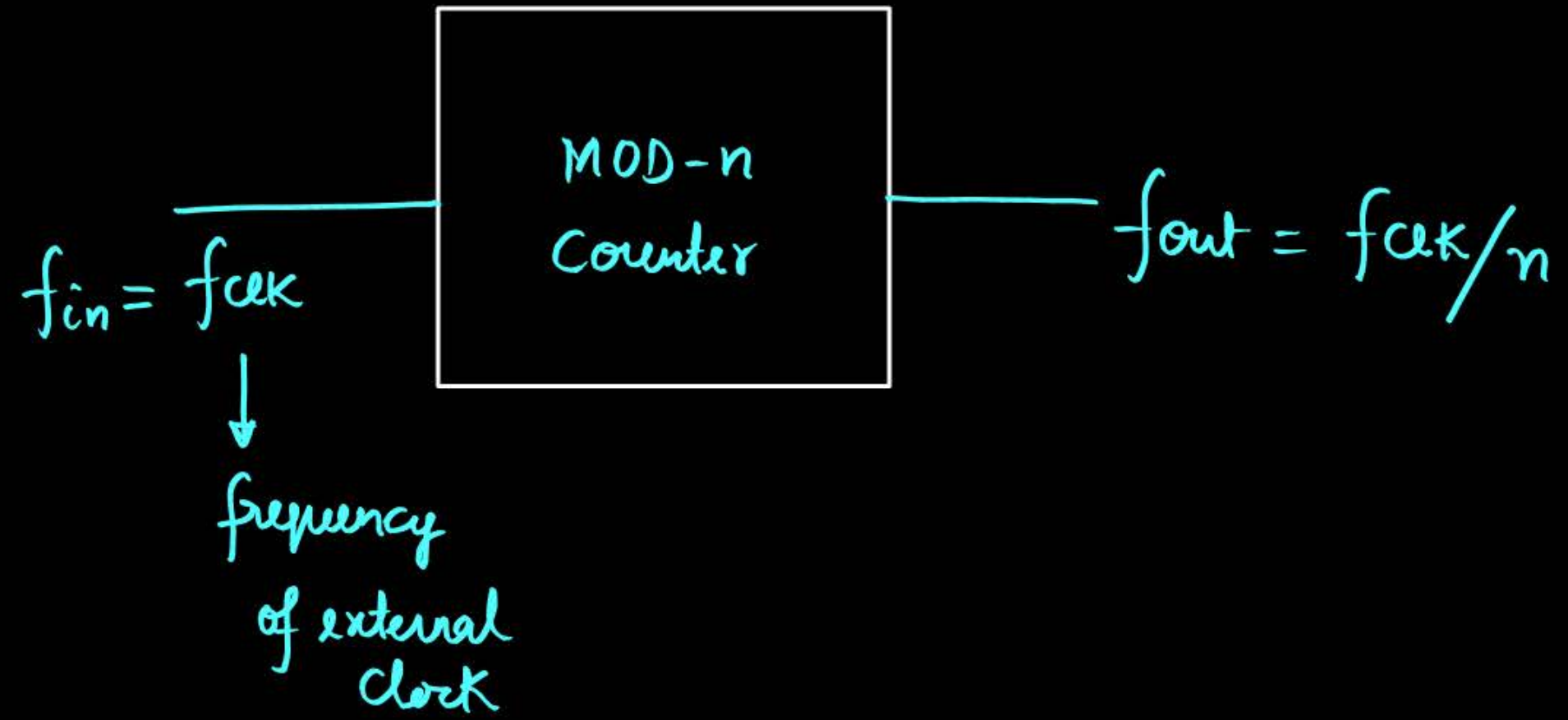
$$(3)_{10} \xrightarrow[260]{65 \times 4} (3)_{10} \xrightarrow{261} 2 \xrightarrow{262} 0 \xrightarrow{263} 1$$








• 0 - 1 - 3 - 2

$f_{clk}/4$   
 $Q_1 \quad Q_0$

|   |   |   |
|---|---|---|
|   | 0 | 0 |
| ↑ | 0 | 1 |
| ↑ | 1 | 1 |
| ↑ | 1 | 0 |
| ↑ | 0 | 0 |

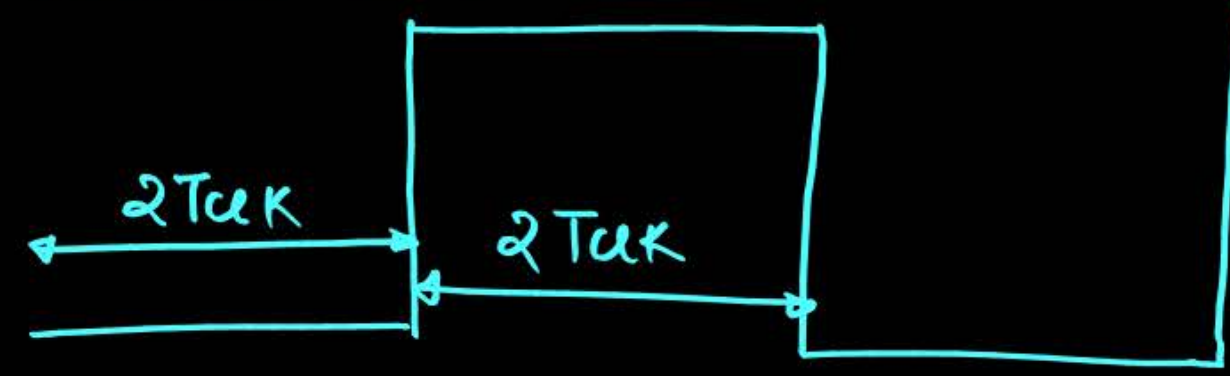MOD no. = 4       $Q_1 \rightarrow T_{ON} = 2T_{clk}, T_{off} = 2T_{clk}$




$$T_{Q_1} = T_{ON} + T_{off} = 4T_{clk}$$

$$f_{Q_1} = \frac{1}{T_{Q_1}} = \frac{1}{4T_{clk}} = \frac{f_{clk}}{4}$$

$Q_0 \rightarrow T_{ON} = 2T_{clk}, T_{off} = 2T_{clk}$

$$T_{Q_0} = T_{ON} + T_{off} = 4T_{clk}$$

$$f_{Q_0} = f_{clk}/4$$

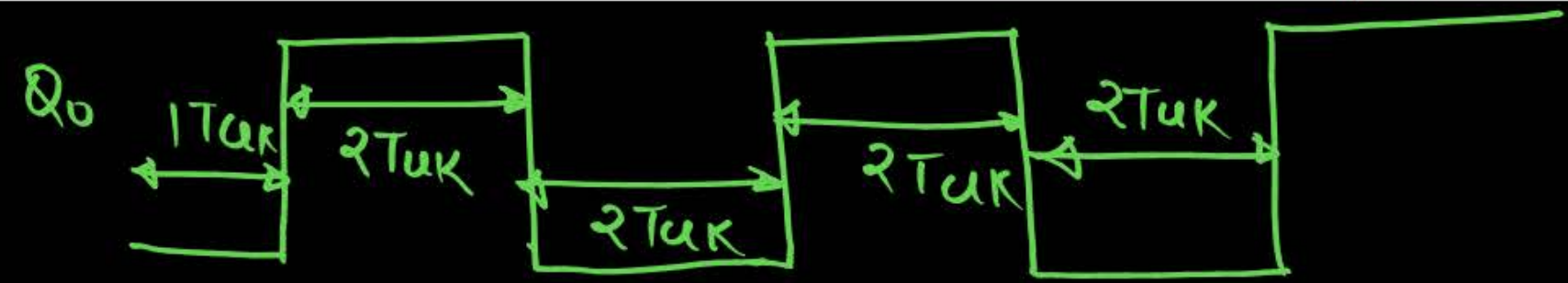

- 0-1-4-3-2-5 MOD no = 6

|                                                                                     | $Q_2$ | $Q_1$ | $Q_0$ |
|-------------------------------------------------------------------------------------|-------|-------|-------|
|                                                                                     | 0     | 0     | 0     |
|    | 0     | 0     | 1     |
|    | 1     | 0     | 0     |
|   | 0     | 1     | 1     |
|  | 0     | 1     | 0     |
|  | 1     | 0     | 1     |

$$Q_0 \rightarrow T_{off} = 1T_{clk}, T_{on} = 1T_{clk}$$

$$T_{Q_0} = 2T_{clk} \quad f_{Q_0} = f_{clk}/2$$

$$Q_1 \rightarrow T_{off} = 4T_{clk}, T_{on} = 2T_{clk}$$

$$T_{Q_1} = 6T_{clk} \rightarrow f_{Q_1} = f_{clk}/6$$

$$Q_2 \rightarrow T_{off} = 2T_{clk}, T_{on} = 1T_{clk}$$

$$T_{Q_2} = 3T_{clk}, f_{Q_2} = f_{clk}/3$$





• 0-1-4-2

MOD no = 4

↳ 3 ff

|     | $Q_2$ | $Q_1$ | $Q_0$ |
|-----|-------|-------|-------|
|     | 0     | 0     | 0     |
| └─┐ | 0     | 0     | 1     |
| └─┐ | 1     | 0     | 0     |
| └─┐ | 0     | 1     | 0     |

$$Q_0 \rightarrow T_{ON} = 1T_{CLK} \quad T_{OFF} = 3T_{CLK}$$


$$T_{Q_0} = 4T_{CLK}, \quad f_{Q_0} = \frac{1}{4} f_{CLK}$$

$$Q_1 \rightarrow T_{ON} = 1T_{CLK}, \quad T_{OFF} = 3T_{CLK}$$

$$T_{Q_1} = 4T_{CLK}, \quad f_{Q_1} = f_{CLK}/4$$

$$Q_2 \rightarrow T_{ON} = 1T_{CLK}, \quad T_{OFF} = 3T_{CLK}$$
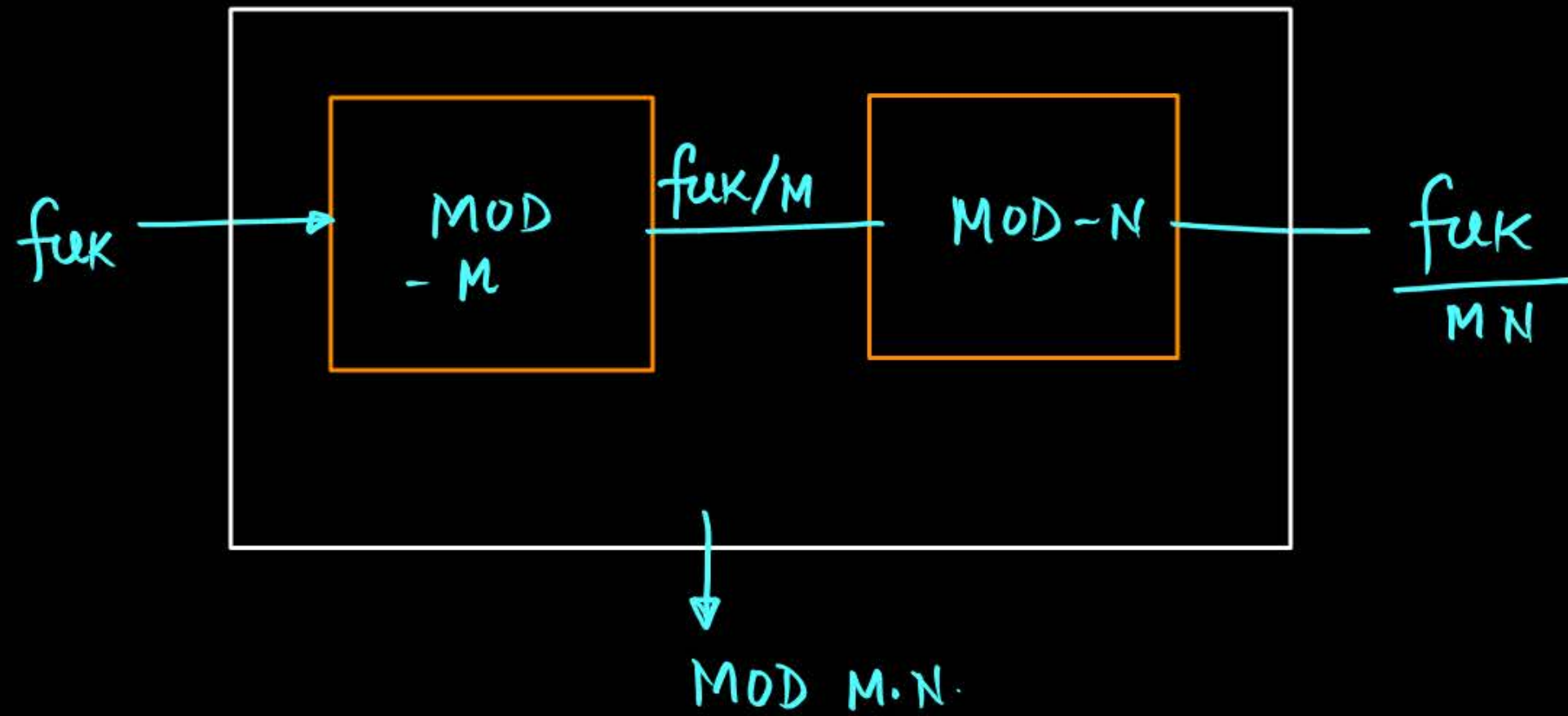
$$T_{Q_2} = 4T_{CLK}, \quad f_{Q_2} = f_{CLK}/4$$



Q. We have a MOD-4 counter and MOD-10 counter cascaded, then what is the resultant MOD no 40.

# [ Types of Counter ]



## Asynchronous Counter

- Here different ffs are driven by different clocks.

- Only fix sequence is possible

up sequence   down sequence

- eg. up counting sequence  
down counting sequence
- It is relatively slower.

## Synchronous Counter

- Here all the ffs are driven by same clock.

- All possible sequences can be designed.

eg. Ring Counter, Johnson Counter etc  
Any sequence.

- It is relatively faster.




# [ 4-bit Asynchronous Counter ]



- Circuit:

condition for asynchronous ff:

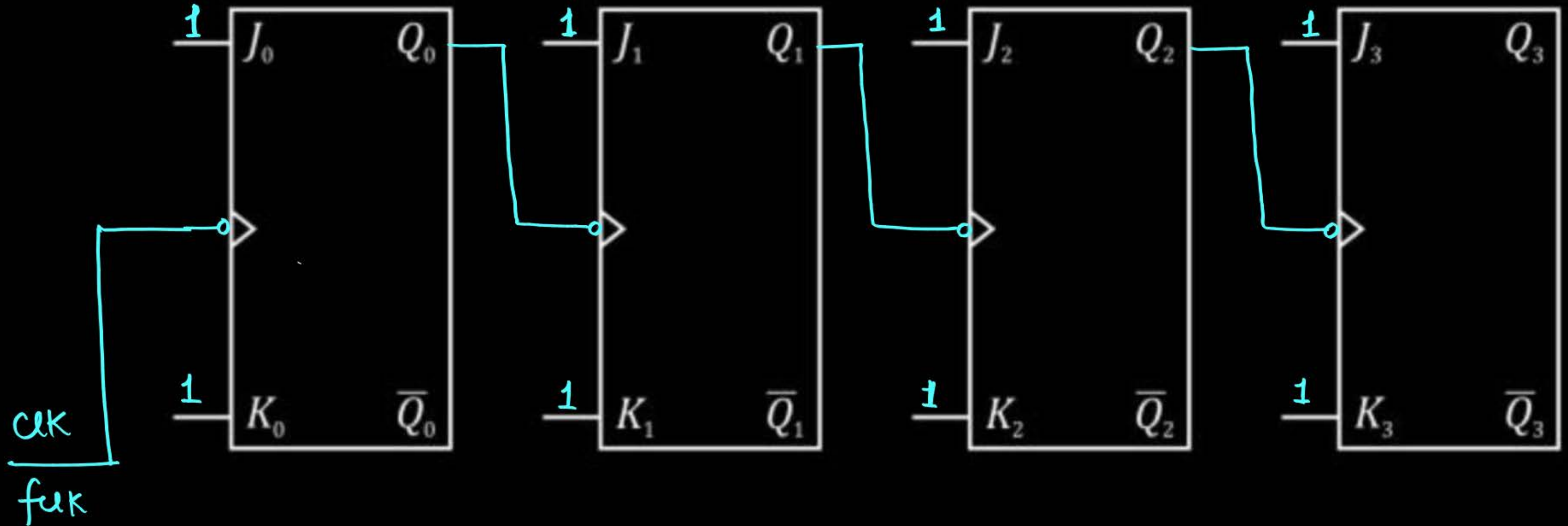1. only one direct clock
2. next ff should trigger by just previous ff
3. should run on toggle mode that is  $j = 1$  and  $k = 1$



- Working:

- $Q_0 \longrightarrow$  toggles in every clock cycle.
- $Q_1 \longrightarrow$  toggles when  $Q_0$  take transition from (1-0).
- $Q_2 \longrightarrow$  toggles when  $Q_1$  take transition from (1-0)
- $Q_3 \longrightarrow$  toggles when  $Q_2$  take transition from (1-0)

# MOD-16 Counter.

Starting state

1<sup>st</sup> clock 

2<sup>nd</sup> clock 

3<sup>rd</sup> clock 

4<sup>th</sup> clock 

5<sup>th</sup> clock

6<sup>th</sup> clock

7<sup>th</sup> clock

8<sup>th</sup> clock

9<sup>th</sup> clock

| $Q_3$ | $Q_2$ | $Q_1$ | $Q_0$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 0     |
| 0     | 0     | 0     | 1     |
| 0     | 0     | 1     | 0     |
| 0     | 0     | 1     | 1     |
| 0     | 1     | 0     | 0     |
| 0     | 1     | 0     | 1     |
| 0     | 1     | 1     | 0     |
| 0     | 1     | 1     | 1     |
| 1     | 0     | 0     | 0     |
| 1     | 0     | 0     | 1     |

$$Q_0 \rightarrow T_{off} = 1T_{clk}, T_{on} = 1T_{clk}$$

$$T_{Q_0} = 2T_{clk} \rightarrow f_{Q_0} = f_{clk}/2$$

$$Q_1 \rightarrow T_{off} = 2T_{clk}, T_{on} = 2T_{clk}$$

$$T_{Q_1} = 4T_{clk}, f_{Q_1} = \frac{f_{clk}}{4}$$

$$Q_2 \rightarrow T_{off} = 4T_{clk}, T_{on} = 4T_{clk}$$

$$T_{Q_2} = 8T_{clk}, f_{Q_2} = \frac{f_{clk}}{8}$$

$$Q_3 \rightarrow T_{off} = 8T_{clk}, T_{on} = 8T_{clk}$$


$$T_{Q_3} = 16T_{clk}, f_{Q_3} = \frac{f_{clk}}{16}$$





|                        |   |   |   |   |
|------------------------|---|---|---|---|
| 10 <sup>th</sup>       | 1 | 0 | 1 | 0 |
| 11 <sup>th</sup>       | 1 | 0 | 1 | 1 |
| 12 <sup>th</sup>       | 1 | 1 | 0 | 0 |
| 13 <sup>th</sup>       | 1 | 1 | 0 | 1 |
| 14 <sup>th</sup>       | 1 | 1 | 1 | 0 |
| 15 <sup>th</sup>       | 1 | 1 | 1 | 1 |
| 16 <sup>th</sup> clock | 0 | 0 | 0 | 0 |

- Clock Diagram :

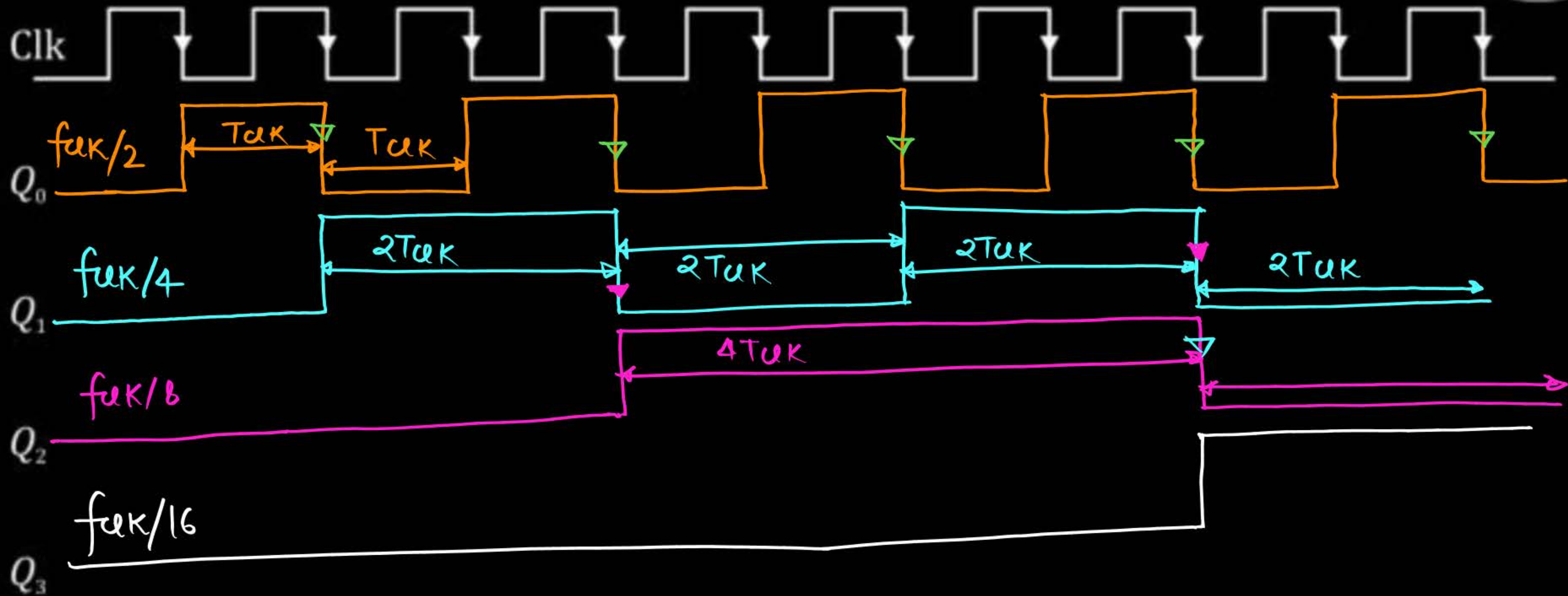



## Topic : 2 Min Summary

→ Asynchronous Counter.



**Thank you**

**GW**  
*Soldiers !*

