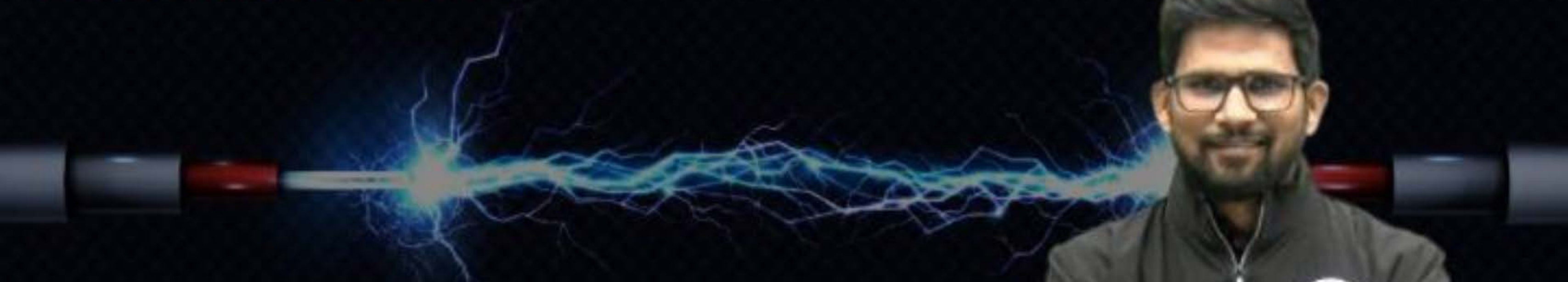




COMPUTER SCIENCE & IT

DIGITAL LOGIC



Lecture No. 03

Combinational Circuit



By- Chandan Gupta Sir



Recap of Previous Lecture

F.A.

Serial adder & Parallel adder



Topics to be Covered

H.S. & F.S.

- To add two n-bit numbers → How many HA's and OR gates required ?

$$1 \text{ H.A.} + (n-1) \text{ F.A.}$$

$$1 \text{ H.A.} + 2(n-1) \text{ HA.} + (n-1) \text{ OR}$$

$$(2n-1) \text{ H.A.} + (n-1) \text{ OR}$$

[Question 4]



To add two 4-bit numbers, minimum number of H.A.s require is m and minimum number of OR gates require is n then value of $(m + n)$ is 10.

$$1HA + 3FA$$

$$= 1HA + 6HA + 3OR$$


$$= 7HA + 3OR$$

$$m = 7HA$$


$$n = 3OR$$

$$m + n = 10$$
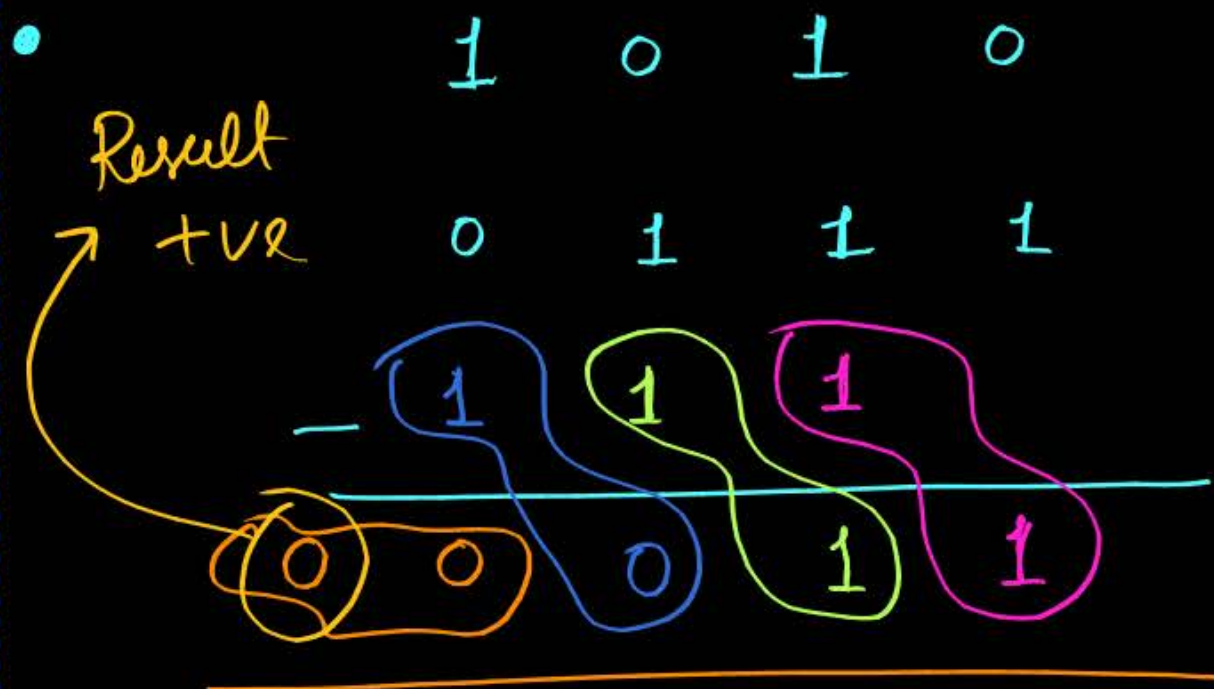
$$\begin{array}{r}
 786 \\
 458 \\
 -01 \\
 \hline
 0328
 \end{array}$$



$$-(00011)$$

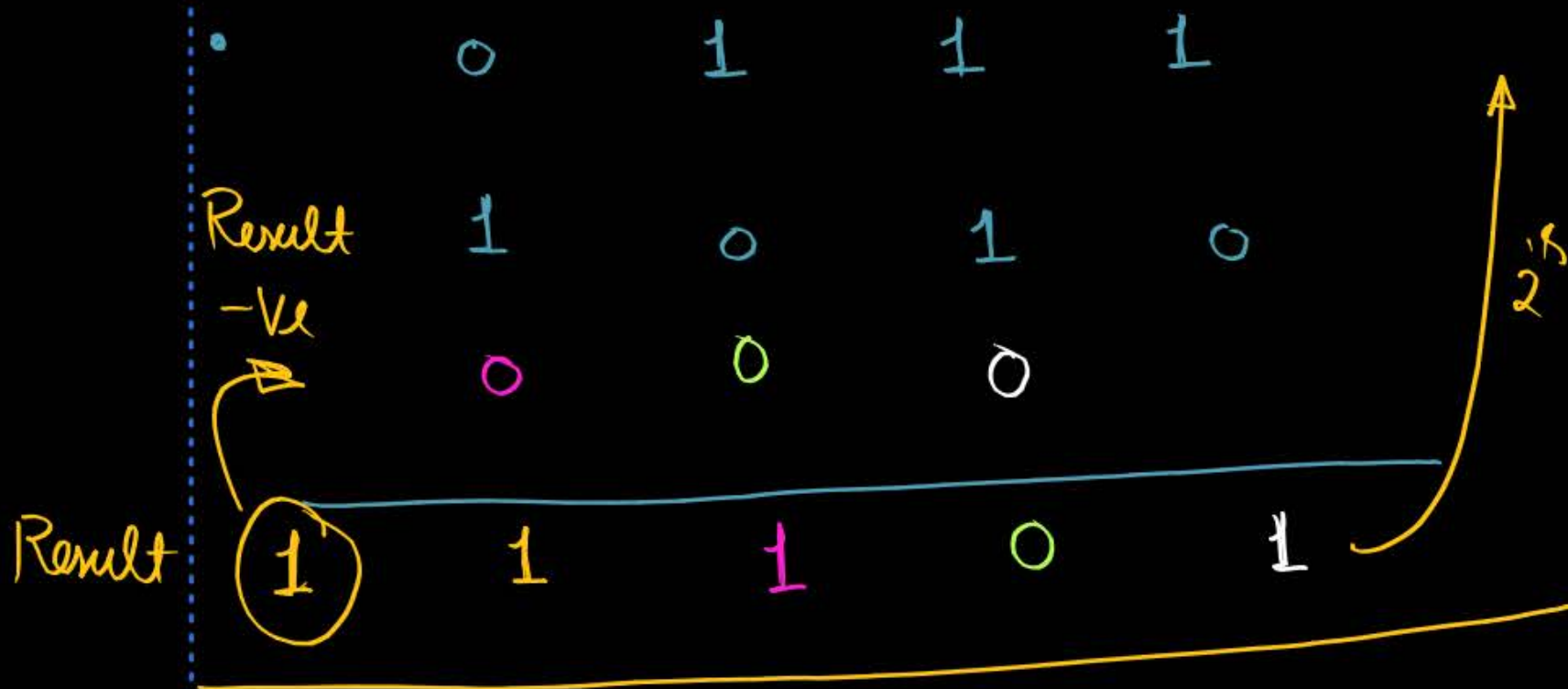



$$\begin{array}{r} 1010 \\ 0001 \\ \underline{001} \\ 01001 \end{array}$$

+9

$$A = \begin{matrix} a_3 & a_2 & a_1 & a_0 \end{matrix}$$
$$B = \begin{matrix} b_3 & b_2 & b_1 & b_0 \end{matrix}$$

$$\begin{array}{r} B_3 \quad B_2 \quad B_1 \\ \hline B_4 \quad D_3 \quad D_2 \quad D_1 \quad D_0 \end{array}$$

$$\begin{array}{r} 0001 \\ 1010 \\ \underline{110} \\ \textcircled{1}0111 \rightarrow \text{Result} \end{array}$$

Result -ve

$$- (2^4 \text{ complement } 10111)$$
$$- (01001)$$
$$- (9)$$

[Half Subtractor]



- What is Half subtractor and what are input lines and what are output lines?

- 2 I/P lines $\rightarrow$ 2 O/P lines $\rightarrow$ $x, y \rightarrow$ corresponding bits of the two no.s
$$\begin{array}{ccc} x \rightarrow a_0 & x \rightarrow a_1 & x \rightarrow a_2 \\ y \rightarrow b_0 & y \rightarrow b_1 & y \rightarrow b_2 \end{array} \text{ etc.}$$
- 2 O/P lines $\rightarrow$ D $\rightarrow$ Difference O/P $\rightarrow$ after considering borrow, the result of subtraction is difference O/P.
B - Borrow O/P $\rightarrow$ Borrow O/P will be '1' if borrow is needed for $x-y$ operation otherwise '0'.

$x - y$

0
1
2
3




Input lines		Output lines	
x	y	D-o/p	B-o/p
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D(x, y) = \sum(1, 2) = \bar{x}y + x\bar{y} = x \oplus y$$


↳ Non self dual

$$B(x, y) = \sum(1) = \bar{x} \cdot y$$

↳ Non-self dual

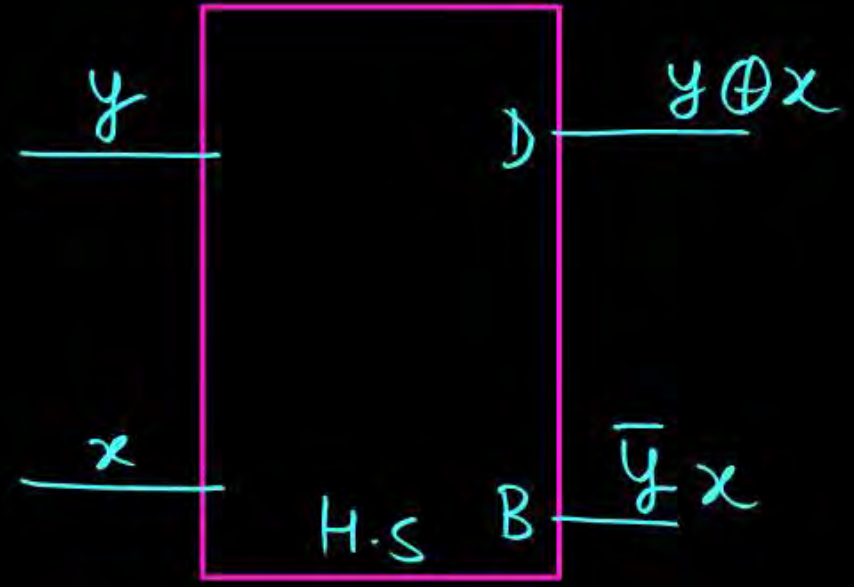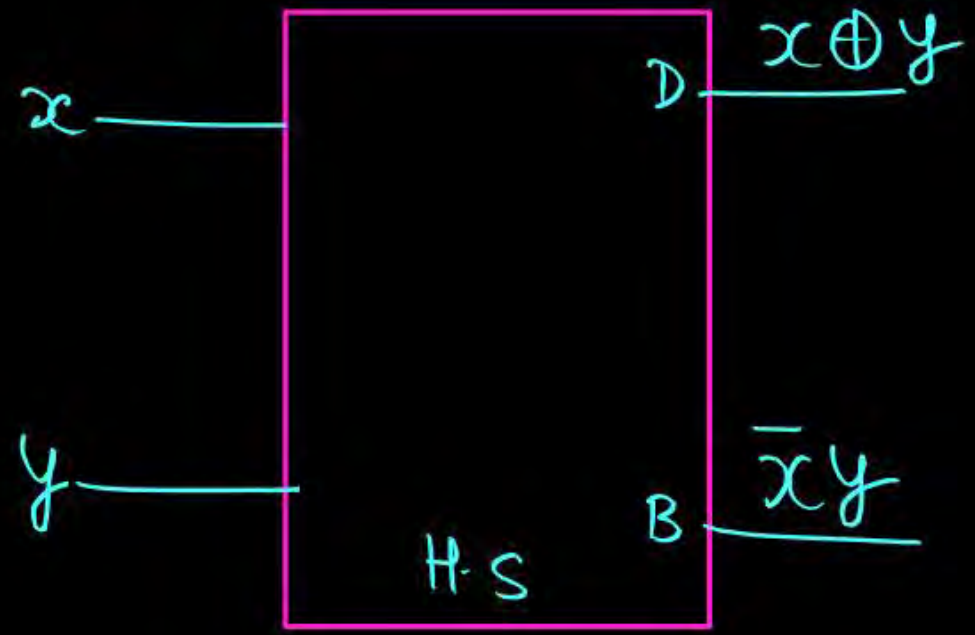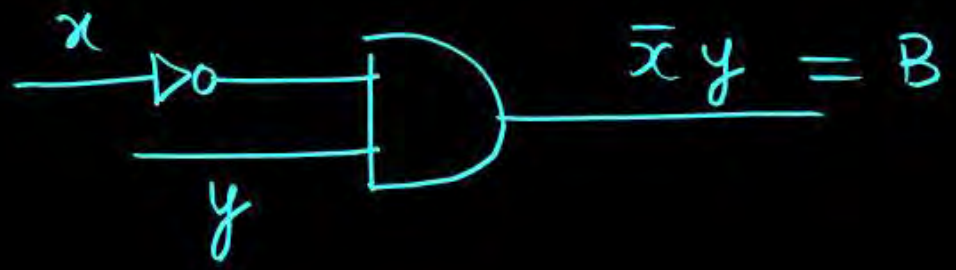


- Using NAND gates : $x-y$

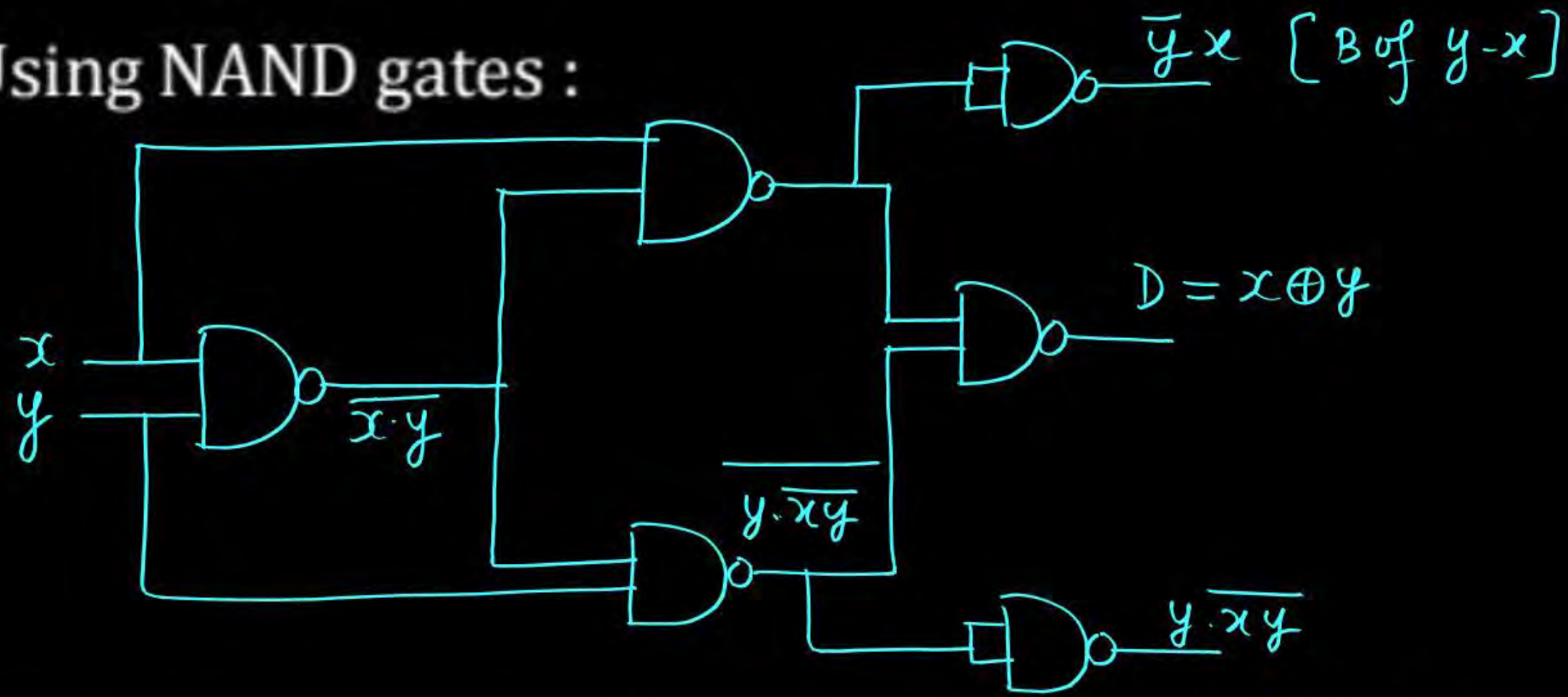

- To implement H.S. we require 5 [2-I/P] NAND gates.

- Using NOR gates :

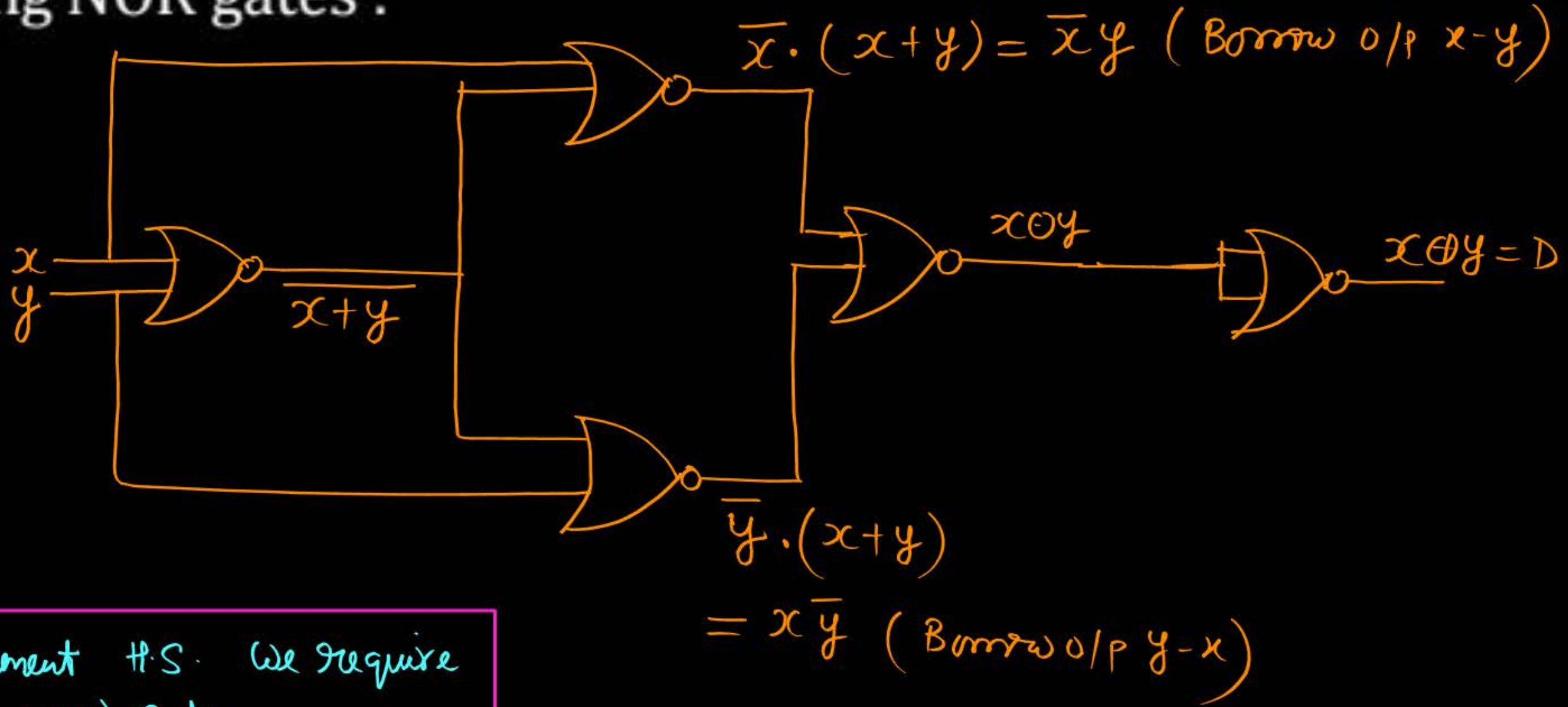

- To implement H.S. we require 5 (2-i/p NOR) gates.

[Full Subtractor]



- What is full subtractor and what are input lines and what are output lines ?

→ I/P lines → 3-I/P lines → x, y → corresponding bits of the two numbers.
 z → borrow I/P from previous subtraction.

x, y → a_1, b_1 then z → B_1 (borrow I/P from a_0, b_0 position)
→ a_2, b_2 then z → B_2 (borrow I/P from a_1, b_1 position)

→ O/P lines → Difference O/P D → after considering borrow, the result of subtraction is difference O/P D .

Borrow O/P → will be '1' if borrow is needed for $x-y-z$ otherwise '0'.

$x-y-z$



Input lines			Output lines	
x	y	z	D-o/p	B-o/p
0	0	0	0	0
1	0	1	1	1
2	0	1	1	1
3	0	1	0	1
4	1	0	1	0
5	1	0	0	0
6	1	1	0	0
7	1	1	1	1

$$y-x-z \rightarrow (x\bar{y} + \bar{y}z + xz) = B$$

$$D(x, y, z) = \sum (1, 2, 4, 7) = \pi (0, 3, 5, 6)$$

Self dual

$$= (x \oplus y \oplus z)$$

$$B(x, y, z) = \sum (1, 2, 3, 7) = \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z$$

Self dual

$$= \bar{x}y + yz + \bar{x}z$$

$$= \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z$$



$$= \bar{x}y + z[\bar{x}\bar{y} + xy] = \bar{x}y + z[\bar{x} \oplus y]$$

$$x+y \rightarrow xy$$


$$x-y \rightarrow \bar{x}y$$

$$x+y+z \rightarrow xy + yz + zx, \quad xy + z[x \oplus y]$$
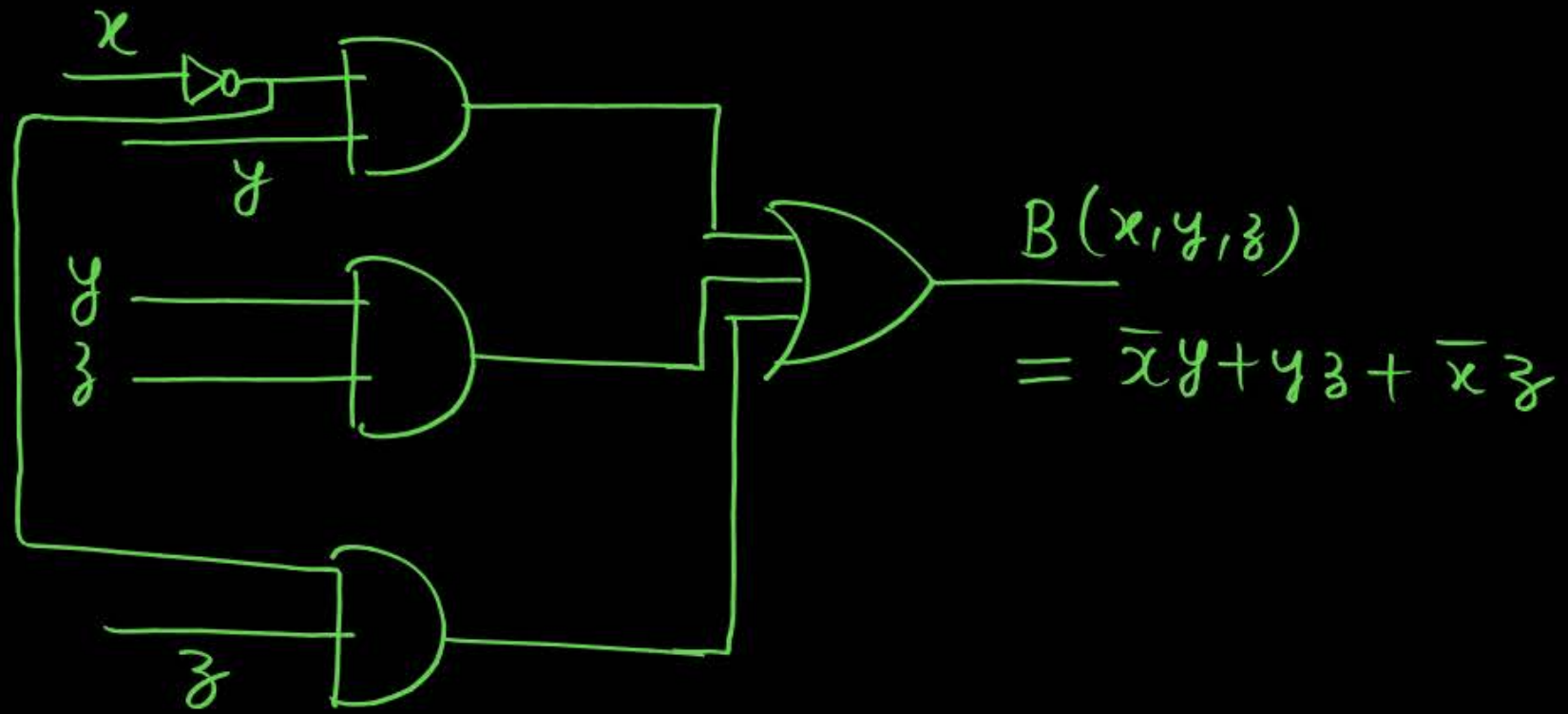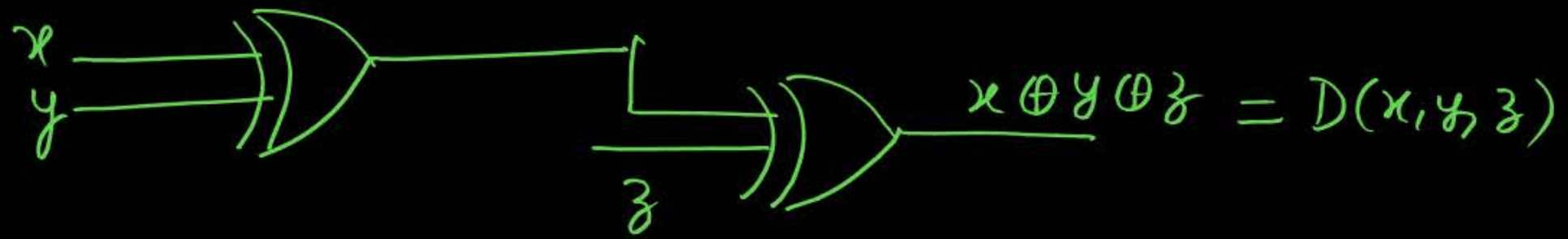
$$x-y-z \rightarrow \bar{x}y + yz + z\bar{x}, \quad \bar{x}y + z[\bar{x} \oplus y]$$



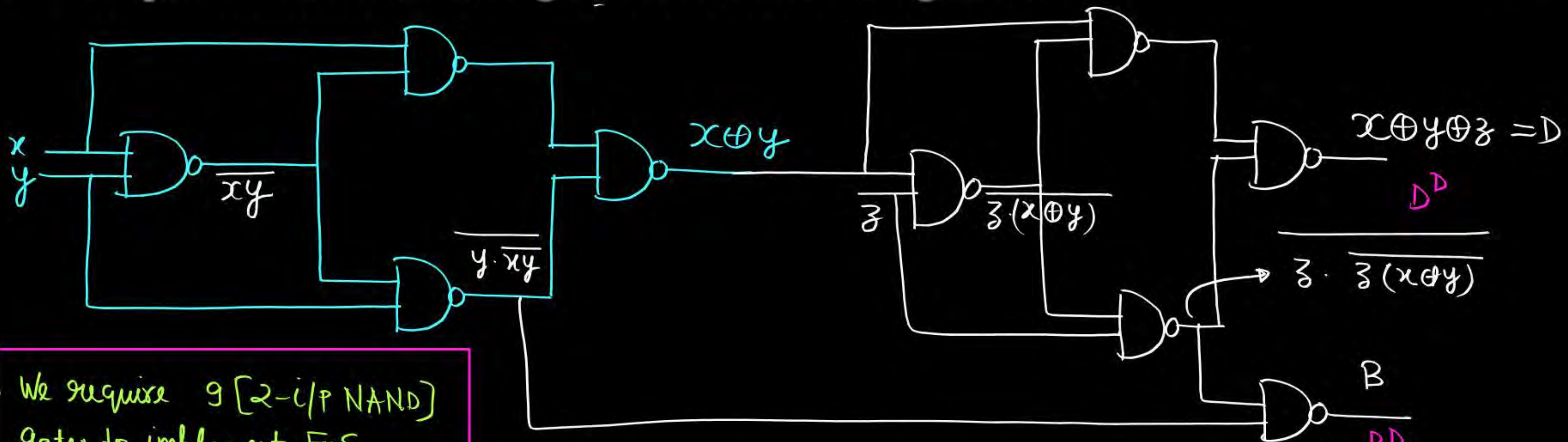- Implementation using NAND and NOR gates :



- We require 9 [2-i/p NAND] gates to implement F.S.


NOR $\rightarrow$ H-W.
(9)

$$\begin{aligned}
 &= y \cdot xy + z \cdot z \cdot (x \oplus y) \\
 &= xy + z \cdot [z + x \oplus y] \\
 &= xy + z[x \oplus y]
 \end{aligned}$$


- Implementation using H.S and OR gate :

$(x-y-z) \rightarrow D = x \oplus y \oplus z$
 $B = \bar{x}y + yz + \bar{x}z = \bar{x}y + z[\bar{x} \oplus y]$

1 FS $\rightarrow$ 2 H.S + 1 OR

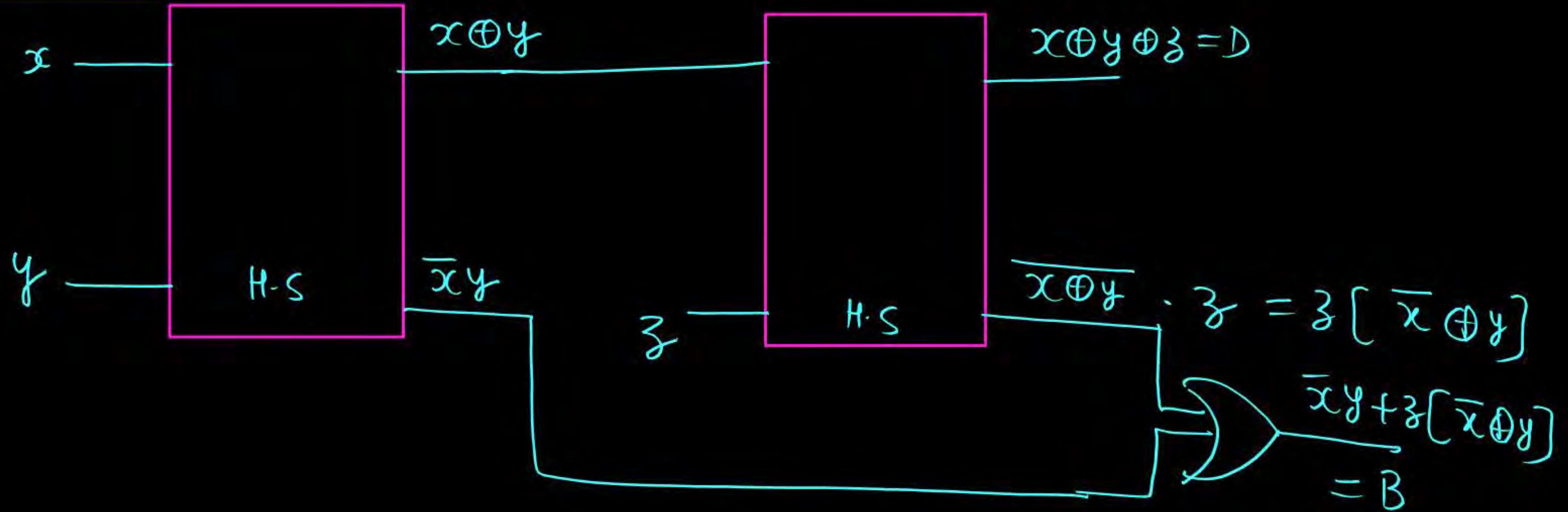

Parallel Subtractor

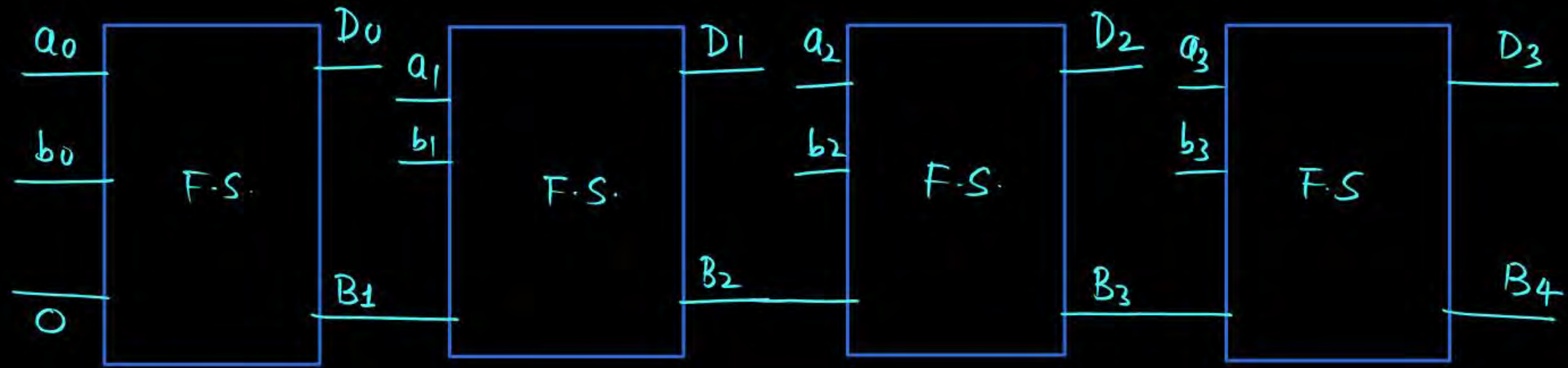

$$\text{Result} = (B_4 D_3 D_2 D_1 D_0)$$

- To subtract two n-bit numbers,, number of H.S. and number of OR gate required is :

$$1 \text{ H.S.} + (n-1) \text{ F.S.}$$

$$1 \text{ H.S.} + 2(n-1) \text{ H.S.} + (n-1) \text{ OR}$$

$$(2n-1) \text{ H.S.} + (n-1) \text{ OR.}$$

[Question]

Two subtract two 4-bit numbers, minimum number of H.S. required is m and minimum number of OR gates require is n then value of $(m + n)$ is 10.

$$1 H.S + 3 F.S.$$

$$1 H.S + 6 H.S + 3 O.R$$

$$= 7 H.S + 3 O.R$$

$$m = 7$$

$$n = 3$$

$$m + n = 10.$$

$$x+y+z \longrightarrow \text{Carry} = xy + yz + zx \\ = xy + (x \oplus y)z$$

$$y+z+x \longrightarrow \text{Carry} = yz + (y \oplus z)x$$

$$z+x+y \longrightarrow \text{Carry} = zx + (z \oplus x)y$$

$$\begin{aligned} \longrightarrow x-y-z &\longrightarrow B = \bar{x}y + yz + \bar{x}z \\ &= \bar{x}y + (\bar{x} \oplus y)z \\ &= yz + (y \oplus z)\bar{x} \\ &= \bar{x}z + (z \oplus \bar{x})y \end{aligned}$$

$$\begin{aligned} \longrightarrow y-x-z &= x\bar{y} + \bar{y}z + xz \\ &= x\bar{y} + (x \oplus \bar{y})z \\ &= \bar{y}z + (\bar{y} \oplus z)x \\ &= xz + (z \oplus x)\bar{y} \end{aligned}$$

$$\begin{aligned} \longrightarrow z-x-y &\longrightarrow x\bar{y} + y\bar{z} + \bar{z}x \\ &\longrightarrow x\bar{y} + (x \oplus y)\bar{z} \\ &\longrightarrow y\bar{z} + (y \oplus \bar{z})x \end{aligned}$$



2 Minute Summary



H.S. & F.S.

Thank you

GW
Soldiers !

