

Electrical Engineering



Electronics and Communication Engineering



Digital Logic



Practice Sheet 01 Discussion
Notes

Combinational Circuits

By- Chandan Gupta Sir

Which of the following is true?

- ☐ **A** All gates follow commutative as well as associative law. ✗
- ☐ **B** NOR & XNOR does not follow associative law. ✗
- ☐ **C** NAND & XOR does not follow associative law ✗
- ☒ **D** All gates follow commutative law but some gates do not follow associative law.


We have to implement half adder as well as half subtractor. Minimum number of 2-i/P NAND gate require is 6.

$$\text{H.A.} \rightarrow S = x \oplus y$$

$$C = x \cdot y$$

$$\text{H.S} \rightarrow D = x \oplus y$$


$$B = \bar{x}y$$

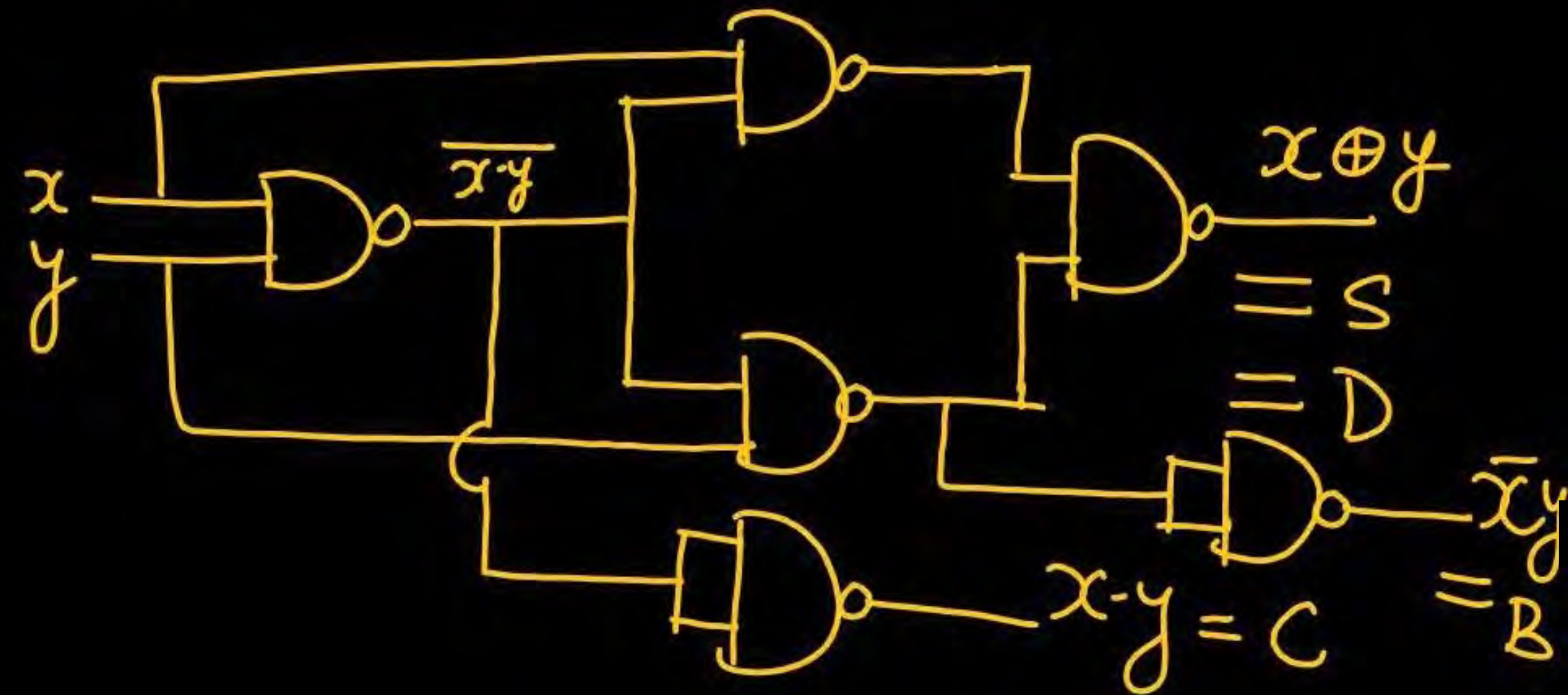

A digital circuit is as given below:

The circuit implements

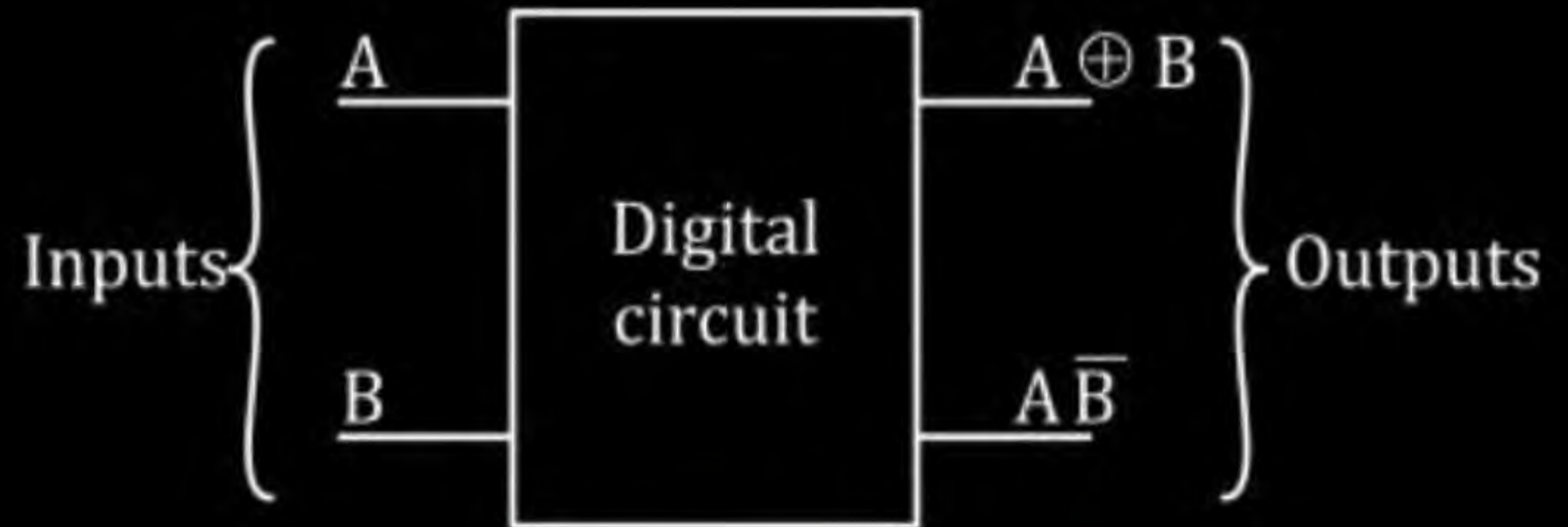- ☐ A $A + B$
- ☐ B $A - B$
- ☒ C $B - A$
- ☐ D None of these



$$A - B \Rightarrow \text{Borrow} = \bar{A} \cdot B$$

$$B - A \Rightarrow \text{Borrow} \Rightarrow \bar{B} \cdot A = A \bar{B}$$

$$y'_1 = (A \oplus B) \oplus \bar{A}B$$

$$= A \oplus B \oplus \bar{A}B = A \oplus [B \cdot \bar{A}B + B \cdot \bar{A}B]$$

$$= A \oplus [B \cdot (A + \bar{A})] = A \oplus [AB]$$

A logical circuit is as given below:


Function of logic circuit - 1 & logic circuit - 2 is same. Then output y'_1 will be

A $A \oplus B$

B $A\bar{B}$

C $\bar{A}B$


D $A - B$

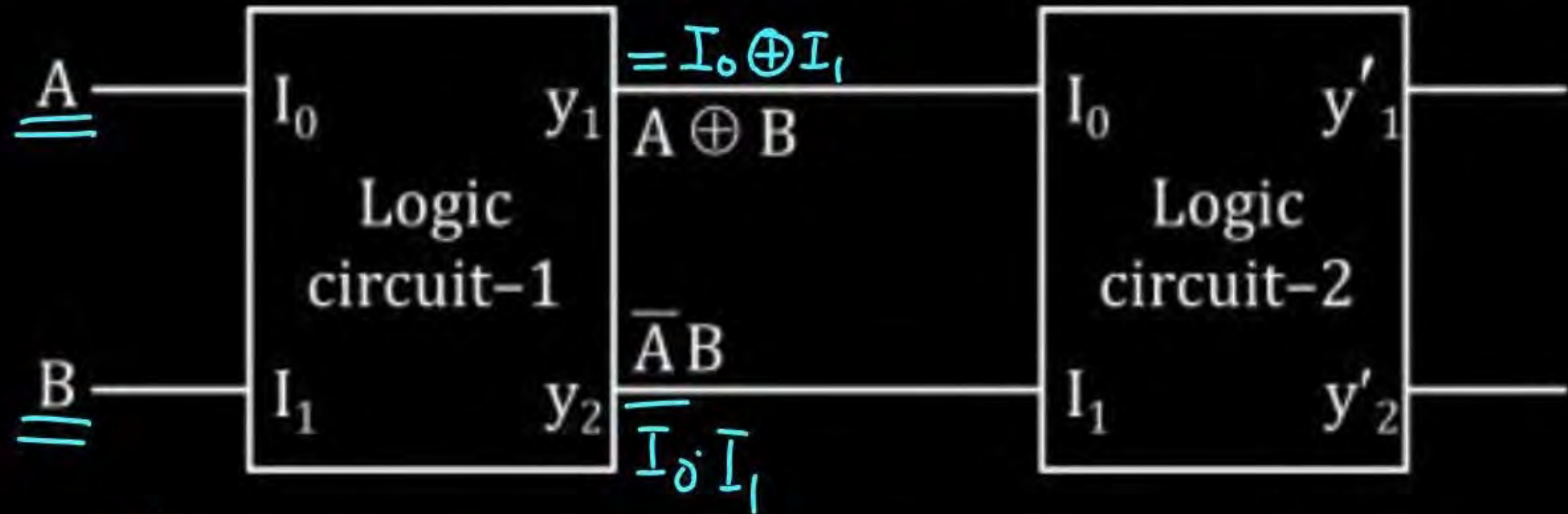

$$y'_1 = A \oplus AB = \bar{A}AB + A \cdot \overline{AB} = A \cdot [\bar{A} + \bar{B}] = 0 + A\bar{B} = A\bar{B}$$


We have two numbers A and B and both are 4-bit numbers. To perform complete addition of these two numbers, total number of H.A.s + OR gate require is 10.

N-bit
 $(2N-1)$ H.A.
 $(N-1)$ OR

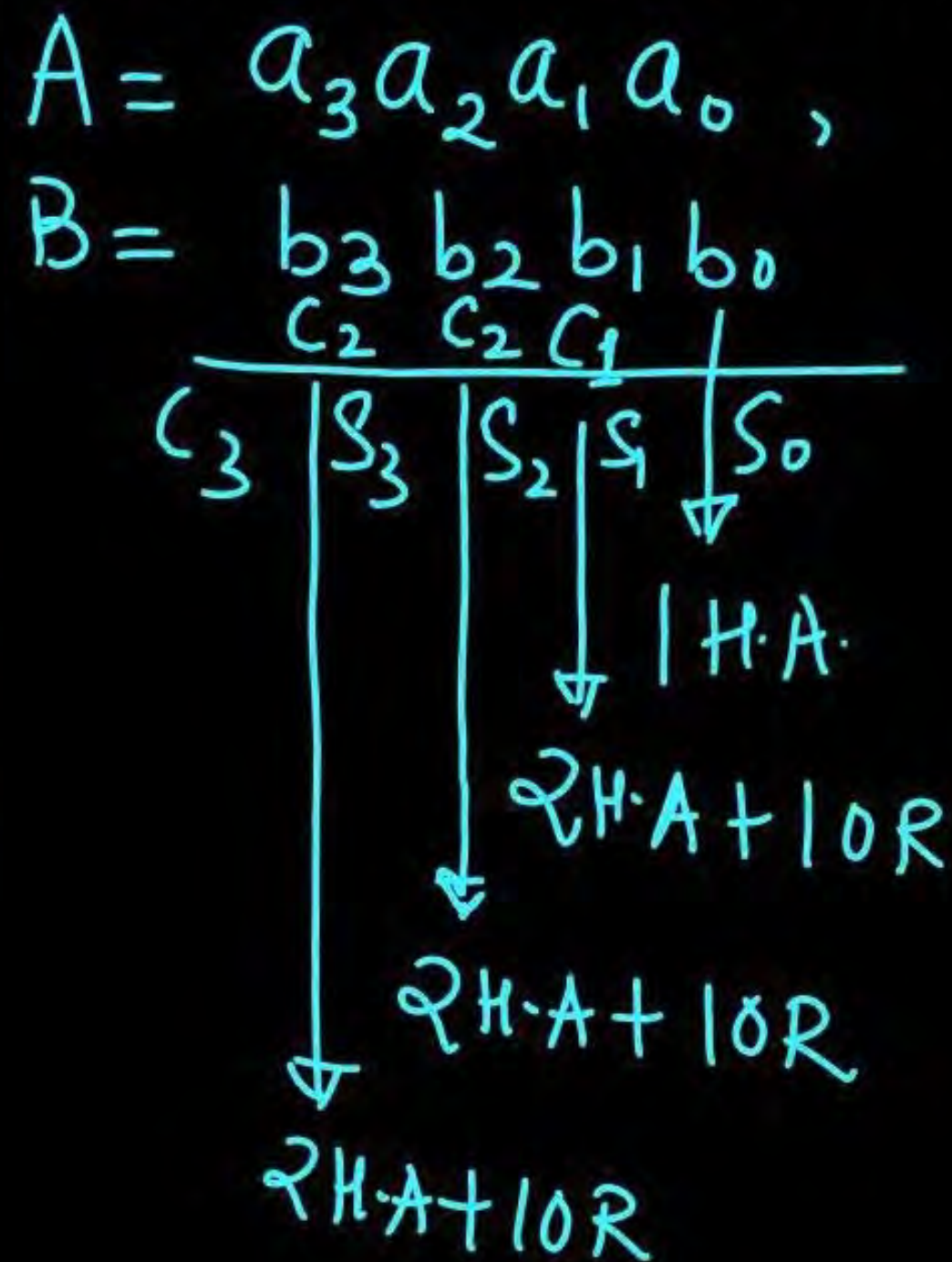

H.A.s $n = 7$ H.A.
 OR gate $m = 3$ OR
 $n + m = 7 + 3 = 10$

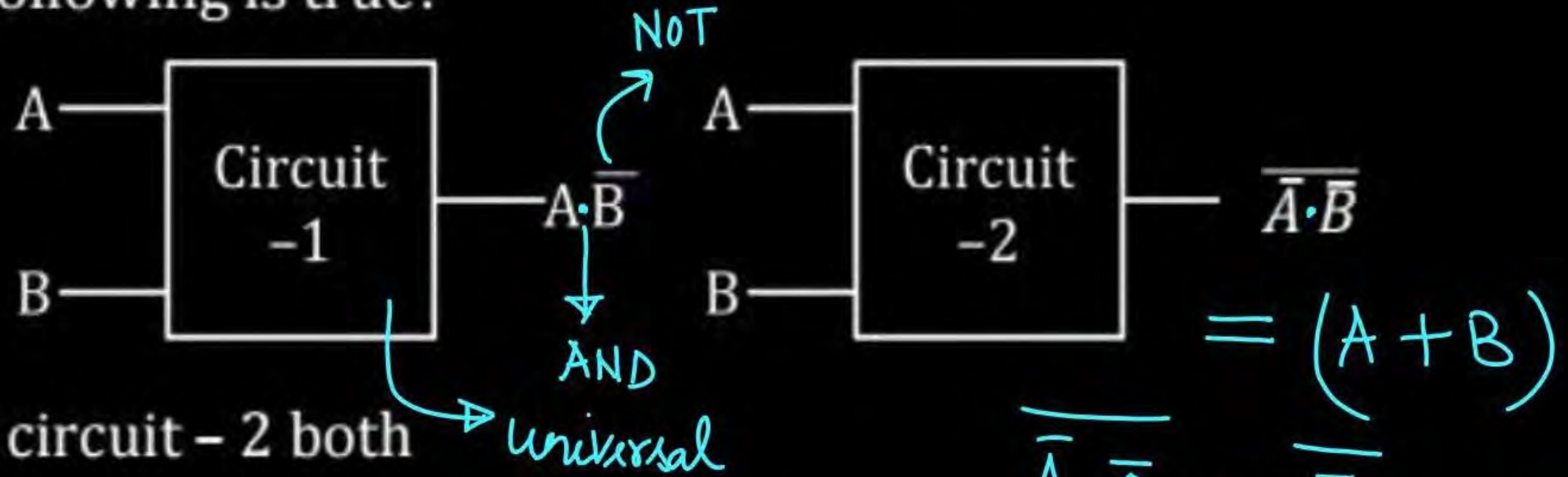
Which of the following circuits can be used as universal circuit :
Then which of the following is true?



- ☒ **A** circuit - 1 and circuit - 2 both
- ☐ **B** circuit - 1 only
- ☐ **C** circuit - 2 only
- ☐ **D** Neither circuit - 1 nor circuit - 2

$$\begin{aligned} \overline{\overline{A} \cdot \overline{0}} &= \overline{\overline{A}} = A \\ \overline{\overline{A} \cdot \overline{1}} &= \overline{0} = 1 \\ \overline{\overline{A} \cdot \overline{A}} &= \overline{\overline{A}} = A \end{aligned}$$

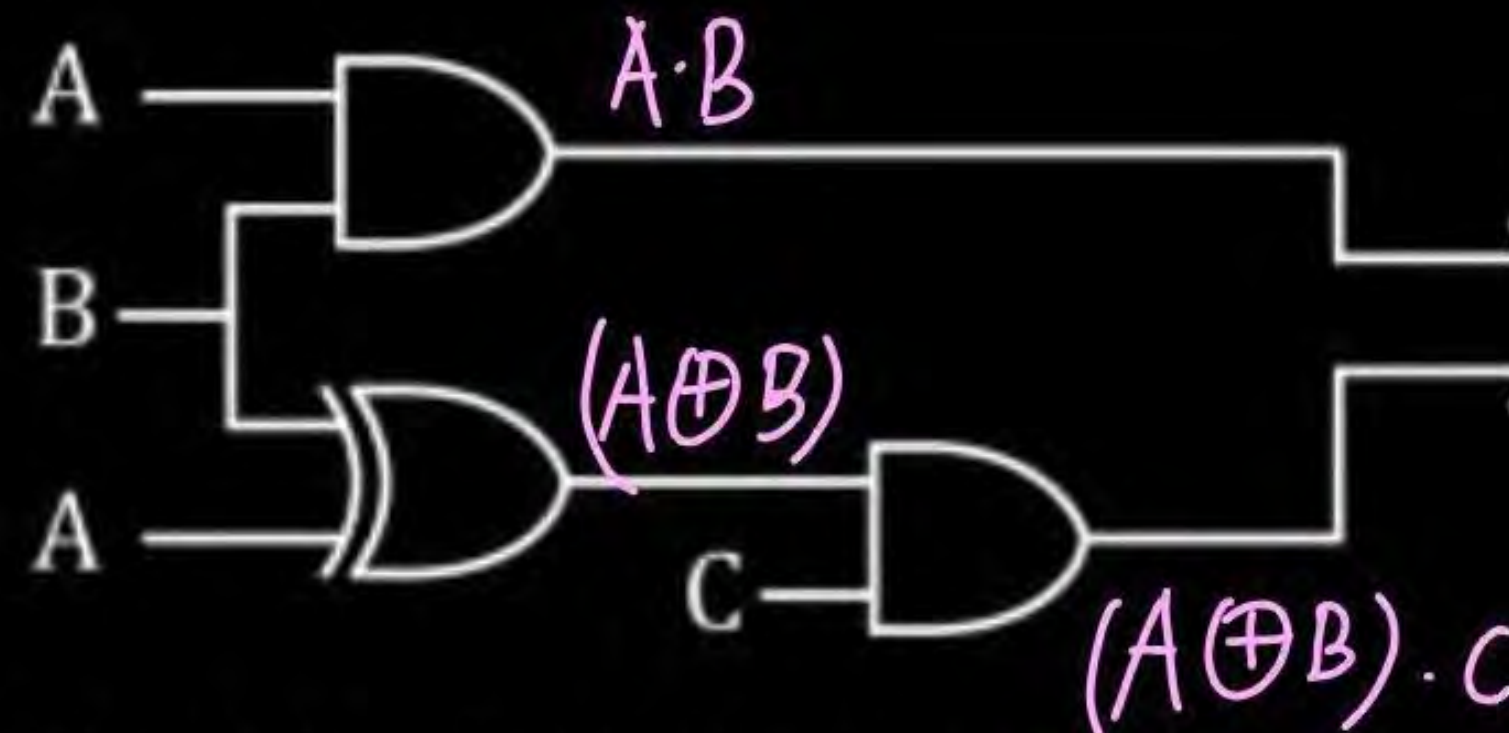A logical circuit is implemented as: (A, B)
Output y is



$$y = \underline{AB} + (A \oplus B)C$$

Carry o/p = $AB + BC + CA$

☒ **A** '1' when majority of the i/Ps A, B, C are at '1'

☒ **B** '0' when minority of the i/Ps A, B, C are at '1'

☒ **C** '1' when minority of the i/Ps A, B, C are at '1'

☒ **D** '0' when majority of the i/Ps A, B, C are at '1'

A	B	C
1	0	0
0	1	0
0	0	1
0	0	0

x, y, z are i/Ps of a full adder then, sum output of full adder will be '1' if

$$\text{Sum} = x \oplus y \oplus z = \Sigma(1, 2, 4, 7)$$

A $\bar{x}\bar{y} + \bar{y}\bar{z} + \bar{z}\bar{x} = 1$ ✗

B $xyz = 1$ ✗

C $(x+y)(y+z)(z+x) = 0$ ✗

D ✓ None of these

Sum=1 ← { only one '1' & two zeros
all 3 i/p are at 1.

$$\overline{(x+y) \cdot (y+z) \cdot (z+x)} = 0$$

$$\overline{(x+y)} + \overline{(y+z)} + \overline{(z+x)} = 1$$

$$(\bar{x} \cdot \bar{y}) + (\bar{y} \cdot \bar{z}) + \bar{z} \cdot \bar{x} = 1$$

Which of the following is/are true?




$$= A + B$$

A NOR gate is equivalent to NAND gate with bubbled i/Ps. $\times$

B OR gate is equivalent to NAND gate with bubbled i/Ps.

C AND gate is equivalent to NOR gate with bubbled i/Ps.

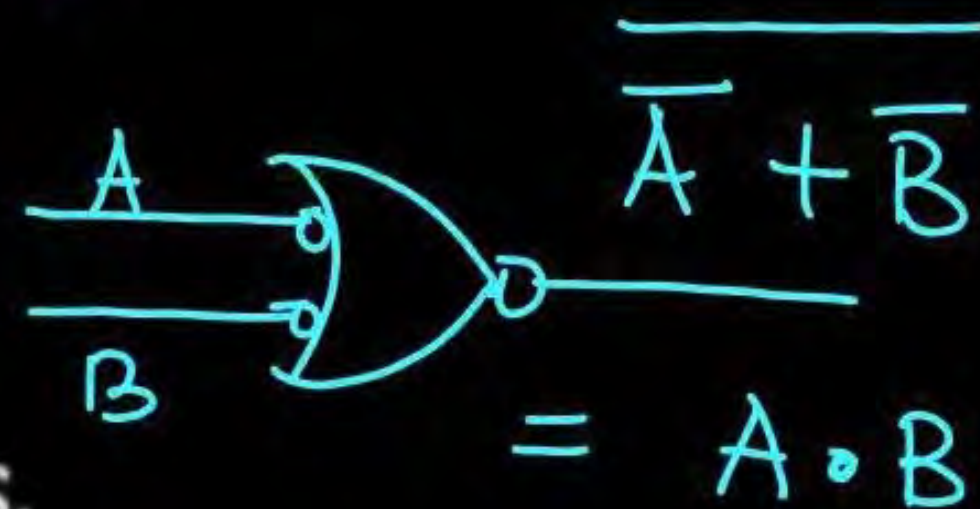D $\times$ NAND gate is equivalent to NOR gate with bubbled i/Ps.



$$= A \cdot B$$


We have to implement H.A circuit & full adder circuit together. i/P lines for H.A. is x, y and i/P lines for full adder is x, y, z then minimum number of 2 - i/P NAND gate require is 10.

$$H.A \rightarrow S_{H.A} = x \oplus y$$

$$C_{H.A} = xy$$

$$F.A \rightarrow S_{F.A} = x \oplus y \oplus z$$
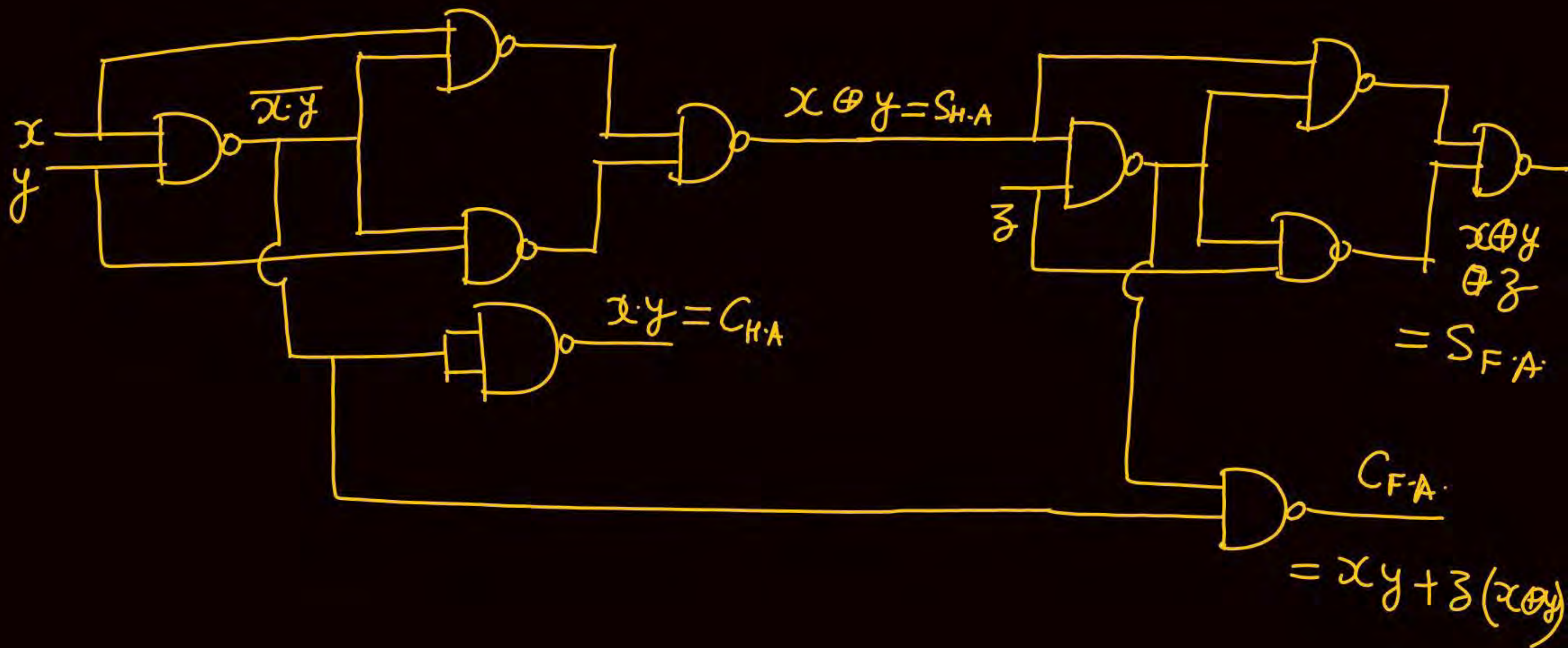
$$C_{F.A} = xy + (x \oplus y) \cdot z = xy + yz + zx.$$



We have a 4-bit adder in which each full adder has sum delay of $t_s = 4 \text{ nsec}$ and carry delay of 2 nsec . In one minute number of additions completed by this full adder is 6×10^9

$$t_s = 4 \text{ nsec}, t_c = 2 \text{ nsec}$$


$$\text{Worst case delay } t_w = (n-1)t_c + \max[t_c, t_s] = 3t_c +$$

$$\therefore 1 \text{ addition is performed in } 10 \text{ nsec} = 3 \times 2 + \max(2 \text{ ns}, 4 \text{ ns}) = 10 \text{ nsec} \quad \text{max}(t_c, t_s)$$

$$\therefore \text{no. of addition performed in one } = \frac{1 \text{ sec}}{10 \text{ nsec}} = \frac{10^9}{10} = 10^8 \text{ additions}$$

$$\therefore \text{no. of addition in 1 minute (60 sec)} = 60 \times 10^8 = 6 \times 10^9 \text{ additions}$$

A logical circuit is as given below:

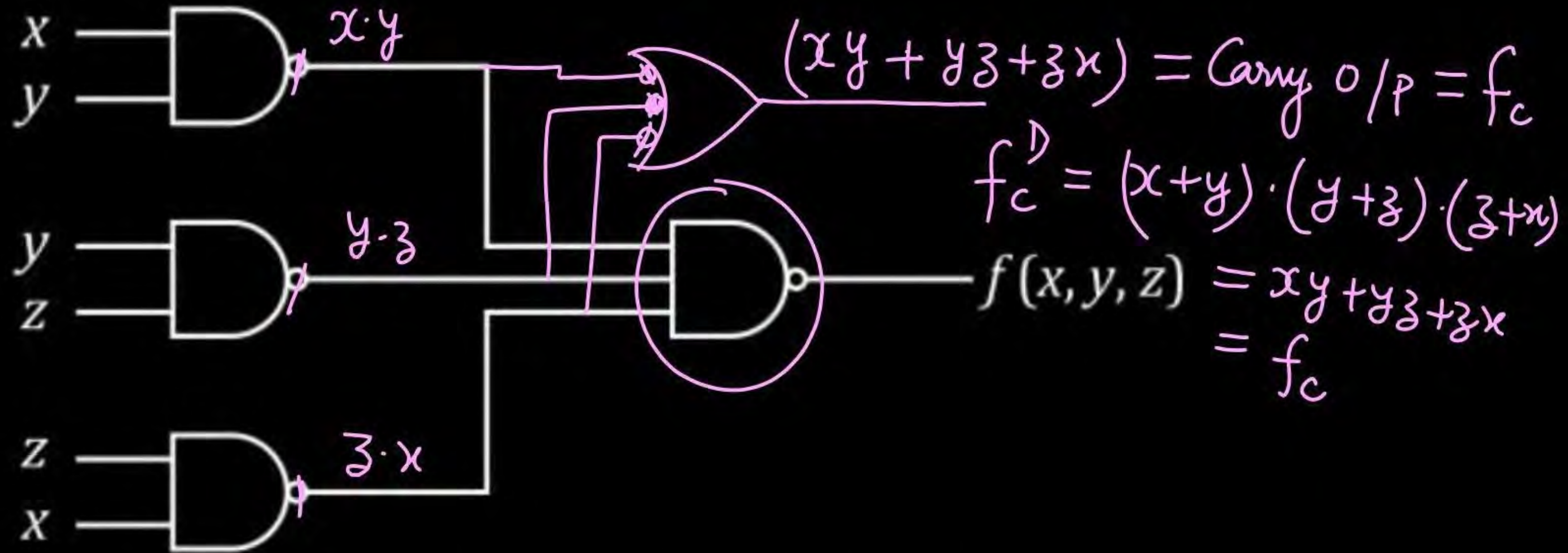


Which of the following circuit is/are equivalent to the above circuit:



i/p y, z, x previous bit generated carry $= yz + zy + xy$


A

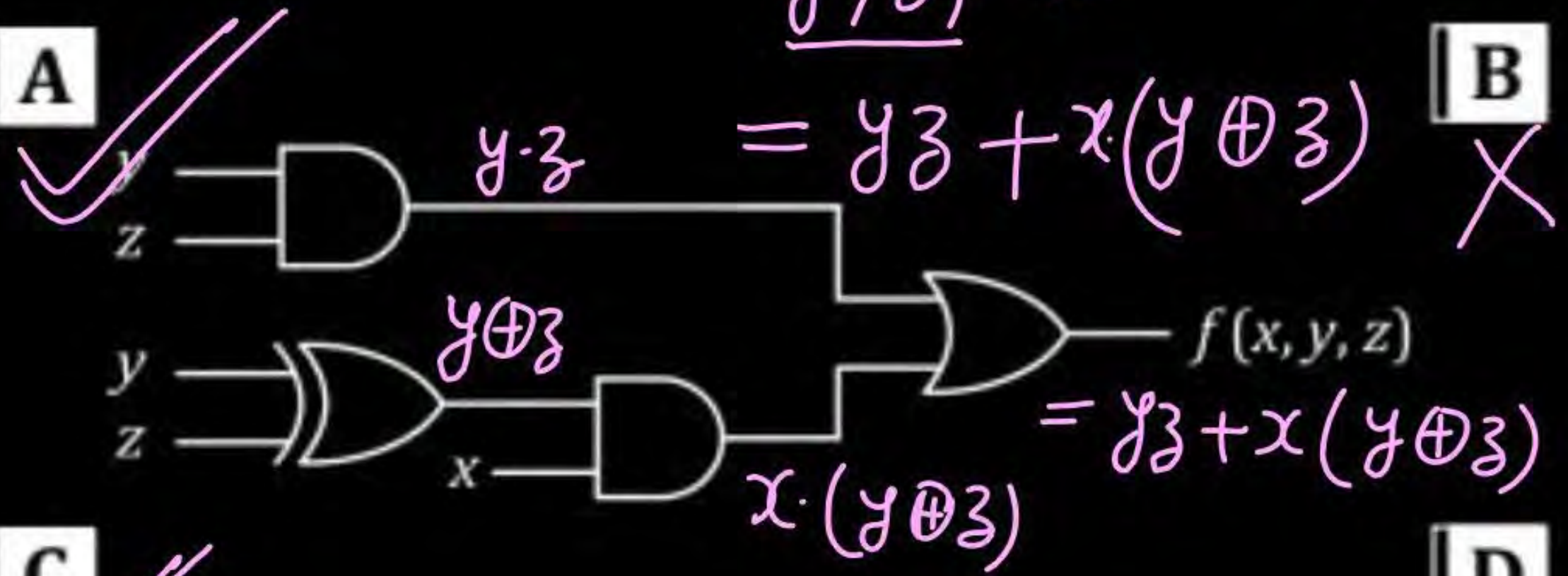


B




C

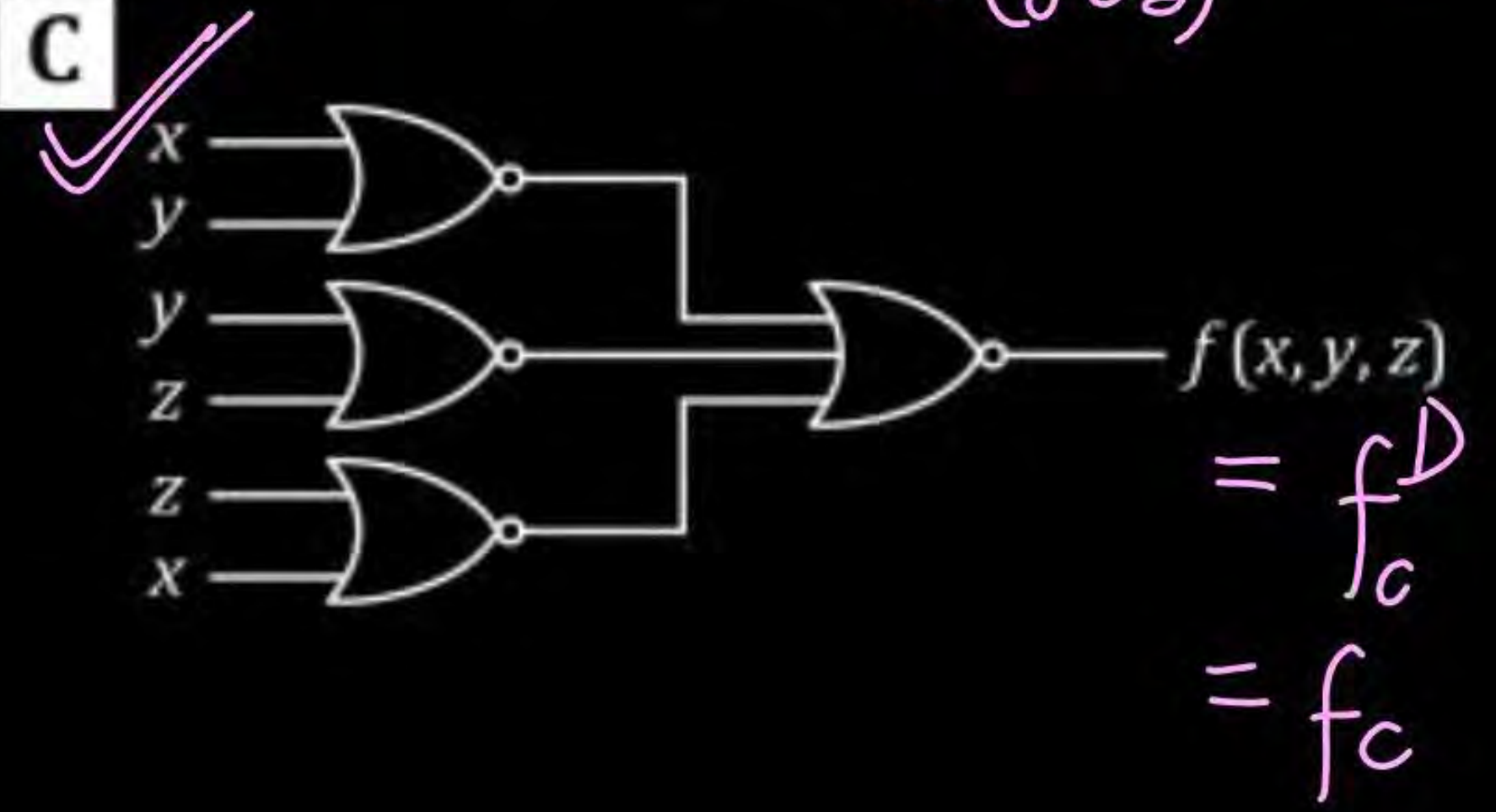

D

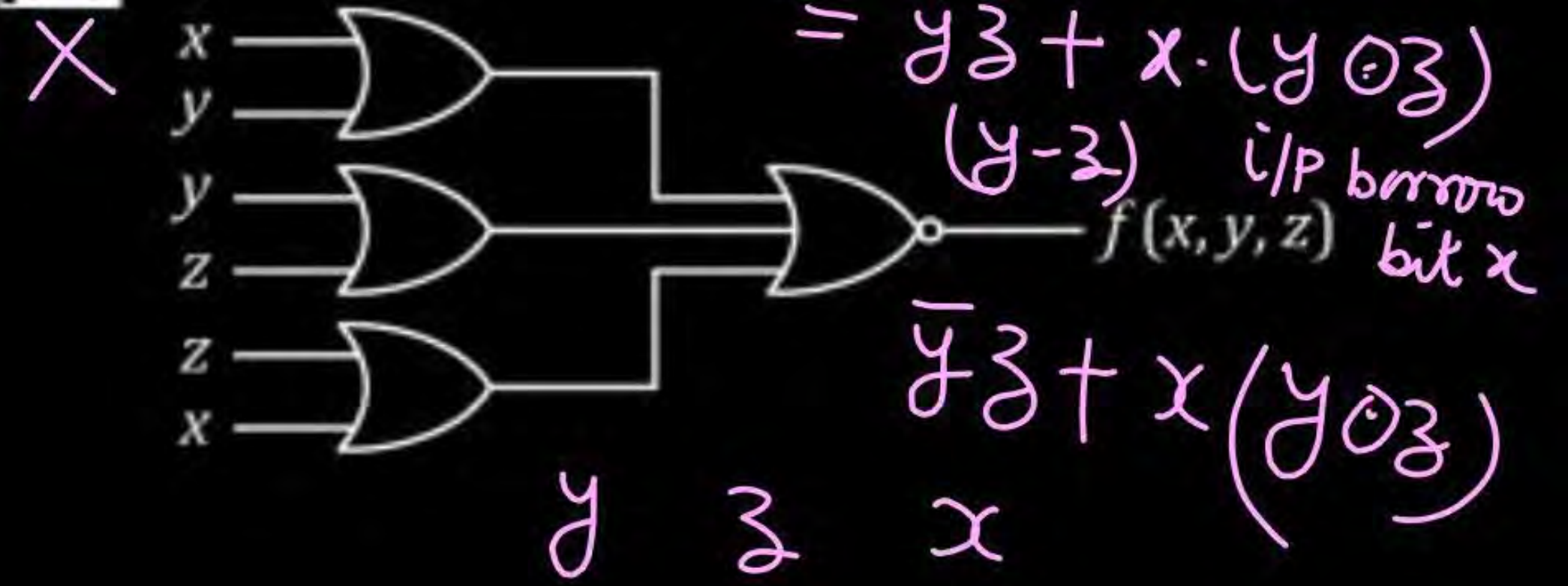

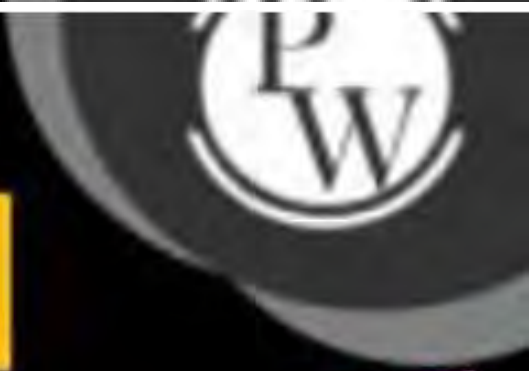

A K-map is as given below :

In minimized solution of above K-map, there are terms $\bar{x}\bar{y}$, $\bar{x}\bar{z}$ and one term is missing. The missing term is

	$\bar{y}\bar{z}$	$\bar{y}z$	yz	$y\bar{z}$
$\bar{x}$	1	1		1
x		1	1	

Handwritten annotations on the K-map:
 - A blue box around the 1s in the first row ($\bar{x}$) is labeled $\bar{x}\bar{y}$.
 - A pink box around the 1s in the first column ($\bar{y}\bar{z}$) is labeled $\bar{x}\bar{z}$.
 - A pink box around the 1s in the third and fourth columns (yz and $y\bar{z}$) for the x row is labeled xz .

A $\bar{y}z$

C $\bar{x}z$

B xz

D $\bar{y}\bar{z}$

	$\bar{y}\bar{z}$	$\bar{y}z$	yz	$y\bar{z}$
$\bar{x}$	1	1		1
x		1	1	

Handwritten annotations on the K-map:
 - A blue box around the 1s in the first row ($\bar{x}$) is labeled $\bar{x}\bar{y}$.
 - A pink box around the 1s in the first column ($\bar{y}\bar{z}$) is labeled $\bar{x}\bar{z}$.
 - A pink box around the 1s in the third and fourth columns (yz and $y\bar{z}$) for the x row is labeled xz .

Handwritten notes:
 $\bar{x}\bar{z}, xz, \bar{y}z$
 or $\bar{x}\bar{z}, xz, \bar{x}\bar{y}$

MCQ

A K-Map is as given below:

	$\bar{y}\bar{z}$	$\bar{y}z$	yz	$y\bar{z}$
$\bar{x}$	1	1		X
x	X		1	1

Handwritten annotations on the K-Map:

- A blue rectangle groups the 1s in the first row ($\bar{x}$), labeled $\bar{x}\bar{y}$.
- A blue oval groups the 1s in the third column (yz), labeled xy .
- A blue oval groups the 1s in the fourth column ($y\bar{z}$), labeled $x\bar{y}$.
- A blue line groups the 1s in the first column ($\bar{y}\bar{z}$), labeled $\bar{z}$.

Its minimized solution will be

$$\begin{aligned} &= \bar{x}\bar{y} + xy \\ &= x \odot y \end{aligned}$$

☒ **A** $x \odot y$

☐ **B** $x \oplus y$

☐ **C** $\bar{z} + \bar{x}\bar{y}$

☐ **D** $\bar{z} + xy + \bar{x}\bar{y}$

MCQ



$$F(x, y, z) = \overline{x\bar{y}} + \bar{x}y + x\bar{y}z + x\bar{y}\bar{z} = \overline{f_1} + x\bar{y}z + x\bar{y}\bar{z}$$

Then the minimized solution of $F(x, y, z)$ will be

$$f_1 = x\bar{y} + \bar{x}y$$

$$F = x + \bar{y}$$

$\overline{f_1}$	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{x}$	1	1	0	0
x	0	0	1	1

F	$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{x}$	1	1		
x	1	1	1	1

$\bar{y}$

x

- ☒ A $x + \bar{y}$
- ☐ B $\bar{x}y$
- ☐ C $xy\bar{z}$
- ☐ D $x + \bar{y} + z$

NAT



In a 4-bit parallel adder, sum delay and carry delay of each full adder is $t_s = 1$ nsec and $t_c = 5$ nsec respectively. Number of additions performed per sec by adder is N_1 . If delays are interchanged then no. of additions performed per sec is N_2 then N_2/N_1 2.5.

$n = 4 \text{ bits} \rightarrow t_s = 1 \text{ nsec}, t_c = 5 \text{ nsec} \rightarrow N_1$

$\therefore \frac{N_2}{N_1} = \frac{10^9/8}{10^9/20} = 2.5$

Worst delay $t_w = (n-1)t_c + \max(t_c, t_s) = 3t_c + \max(5 \text{ nsec}, 1 \text{ nsec})$

$N_1 = \frac{1 \text{ sec}}{t_w} = \frac{1 \text{ sec}}{20 \text{ nsec}} = \frac{1}{20 \times 10^{-9}} = \frac{10^9}{20} \text{ additions in one second}$

$t'_s = 5 \text{ nsec}, t'_c = 1 \text{ nsec} \rightarrow t'_w = 3t'_c + \max(t'_c, t'_s) = 3 \times 1 + \max(1 \text{ nsec}, 5 \text{ nsec}) = 8 \text{ nsec}$

$\therefore N_2 = \frac{1 \text{ sec}}{t'_w} = \frac{1 \text{ sec}}{8 \text{ nsec}} = \frac{10^9}{8} \text{ additions}$

Question

MCQ

A K-map is as given below :

$$= \bar{A}\bar{C} + CD$$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	
$\bar{A}B$	1	1	1	X
AB			1	
$A\bar{B}$		X	X	

Handwritten annotations on the K-map:

- A cyan box highlights the first two columns ($\bar{C}\bar{D}$ and $\bar{C}D$), with an arrow pointing to $\bar{A}\bar{C}$.
- A yellow box highlights the first two rows ($\bar{A}\bar{B}$ and $\bar{A}B$), with an arrow pointing to $\bar{A}D$.
- A pink box highlights the third and fourth rows (AB and $A\bar{B}$), with an arrow pointing to CD .



Then minimized solution of K-map is :

A $\bar{A}\bar{C} + \bar{A}D + CD$ ✗

☒ **B** $\bar{A}\bar{C} + CD$

C $\bar{A}B + CD + \bar{A}\bar{C}$

D None of these

MCQ



K-map of two logical functions $f_1(A, B)$ and $f_2(A, B)$ is as given below :

f_1	$\bar{B}$	B
$\bar{A}$	1 ₀	₁
A	₂	1 ₃

$$f_1(A, B) = \sum (0, 3)$$


$$A=0, B=0$$

$$A=0, B=1$$

f_2	$\bar{B}$	B
$\bar{A}$	1 ₀	1 ₁
A	₂	₃

$$f_2(A, B) = \sum (0, 1)$$

Then K-map of $f(A, B)$ will be

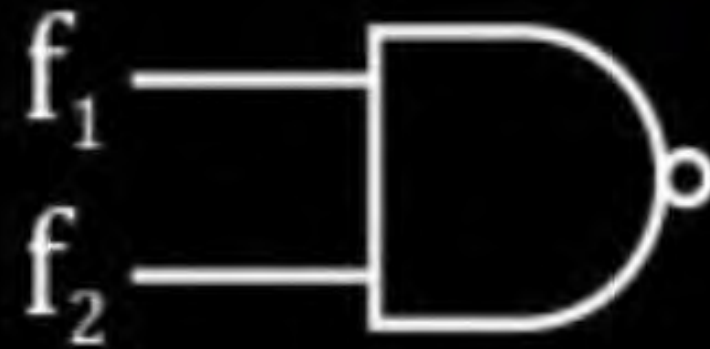

$$f(A, B) = \sum (1, 2, 3)$$

A

f

	$\bar{B}$	B
$\bar{A}$	1	1
A		1

B

f

	$\bar{B}$	B
$\bar{A}$		1
A	1	1

C

f

	$\bar{B}$	B
$\bar{A}$	1	1
A		

D

f

	$\bar{B}$	B
$\bar{A}$		1
A	1	

NAT



$f(A, B, C, D)$ is as given below :

$$f(A, B, C, D) = \overline{B}D + AC + \overline{A}B + ABCD + \overline{A}BC + ABD = \overline{f_1} + ABCD + \overline{A}BC + ABD$$

Then number of entries in K-map of $f(A, B, C, D)$ that are filled with '1' is

8

$f_1 = \overline{B}D + AC + \overline{A}B$

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1			1
$\overline{A}B$			1	1
AB	1	1	1	
$A\overline{B}$	1			

f_1

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	0	0	1
$\overline{A}B$	0	0	0	0
AB	1	1	0	0
$A\overline{B}$	1	0	0	0

Question

MCQ

$f(x, y, z)$ is given as: $f(x, y, z) = \bar{x}\bar{y} + \bar{x}z + xy$,
The equivalent $f(x, y, z)$ can also be

		f			
		$\bar{y}\bar{z}$	$\bar{y}z$	$y\bar{z}$	yz
$\bar{x}$		1 0	1 1	1 3	0 2
x		0 4	0 5	1 7	1 6

A $(\bar{x} + y + \bar{z})(x + \bar{y} + \bar{z})(x + \bar{y} + z)$

B $(x + \bar{y} + z)(\bar{x} + y + z)(\bar{x} + y + \bar{z})$

C $(\bar{x} + \bar{y})(\bar{x} + z)(x + y)$ ✗

D None of these

$f(x, y, z) = \sum (0, 1, 3, 6, 7) = \pi (2, 4, 5)$

$010, 100, 101$

$= (x + \bar{y} + z) \cdot (\bar{x} + y + z)(\bar{x} + y + \bar{z})$

MCQ

Which of the following is true ?

- ☐ **A** K-map has more than one solution. ✗
- ☐ **B** K-map has always unique solution. ✗
- ☒ **C** K-map can have more than one solution.
- ☐ **D** None of these

$$A > B = 1 + 2 + 3 = 6$$

Two no's A & B are two bit no's as

$$A = a_1 a_0 \text{ and } B = b_1 b_0$$

Then no. of combination in which $A > 2B$ 4.

$$A \rightarrow 2 \text{ bit} \rightarrow 0, 1, 2, 3$$

$$B \rightarrow 2 \text{ bit} \rightarrow 0, 1, 2, 3$$

$$2B \rightarrow 0, 2, 4, 6$$

When $A = 0 \rightarrow$ no
Combination


When $A = 1 \rightarrow$ one combination
 $A > 2B$
 $A > 2B$ [when $2B = 0$]

When $A = 2 \rightarrow$ one combination
 $A > 2B$ [$2B = 0$]

When $A = 3 \rightarrow$ two combinations
 $A > 2B$ [$2B = 0, 2B = 2$]

$$\text{Total} = 1 + 1 + 2 = 4$$

A digital ckt is as given below:

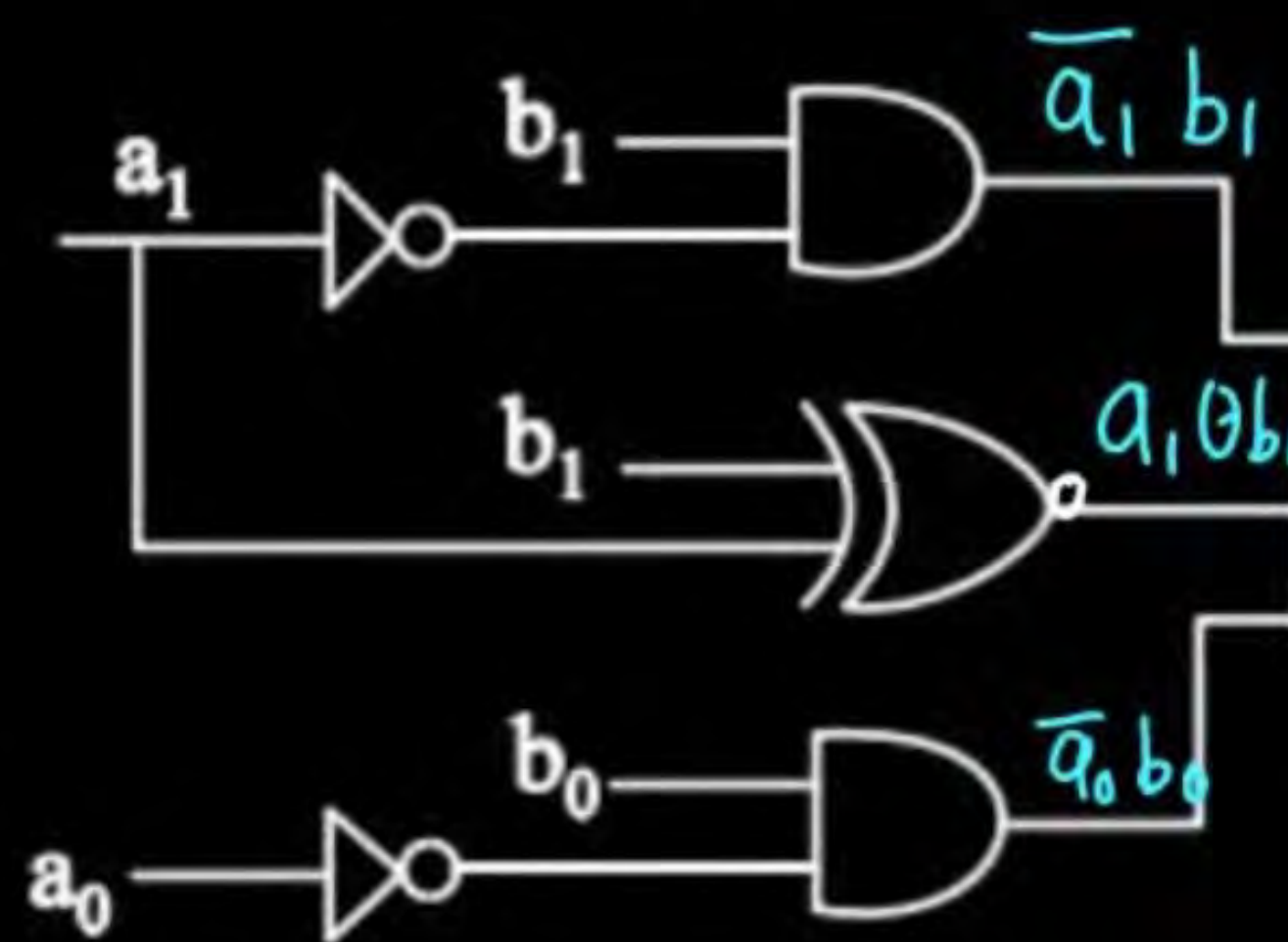

$$A = a_1 a_0$$

$$B = b_1 b_0$$

$$(A < B) = \bar{a}_1 b_1 + (a_1 \oplus b_1) \bar{a}_0 b_0$$

$$= 1 + 2 + (2^2 - 1) = 6$$

$$y = \bar{a}_1 b_1 + (a_1 \oplus b_1) \bar{a}_0 b_0$$

$$A > B = 6$$


$$A = B = 2^n = 4$$

i/p lines of the ckt are a_1, b_1, a_0, b_0 and o/p line is y .

Then no. of combinations of i/p lines in which o/p y will be '1' is 6.

Question

A MUX circuit is as given below:

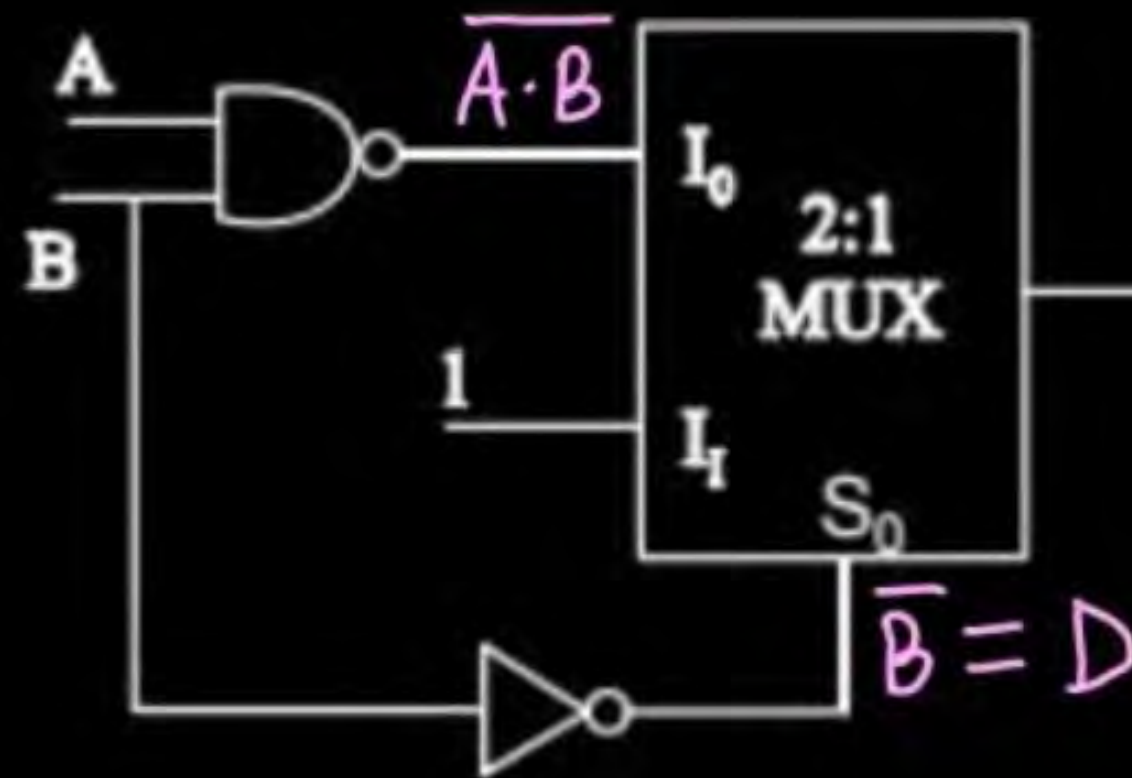

o/p y is.

$$y = \overline{D} \cdot \overline{A \cdot B} + D \cdot 1$$

$$= B (\overline{A} + \overline{B}) + \overline{B}$$

$$= \overline{A} \cdot B + 0 + \overline{B}$$

$$= \overline{A} B + \overline{B} = \overline{B} + (\overline{A} \cdot B)$$

$$= (\overline{B} + \overline{A}) \cdot (\overline{B} + B) = (\overline{A} + \overline{B})$$

$$= \overline{A \cdot B}$$


☒ **A** $\overline{A} + \overline{B}$

☐ **B** $\overline{A + B}$

☐ **C** $A \oplus B$

☐ **D** $A \overline{B}$

A MUX ckt is as given below:

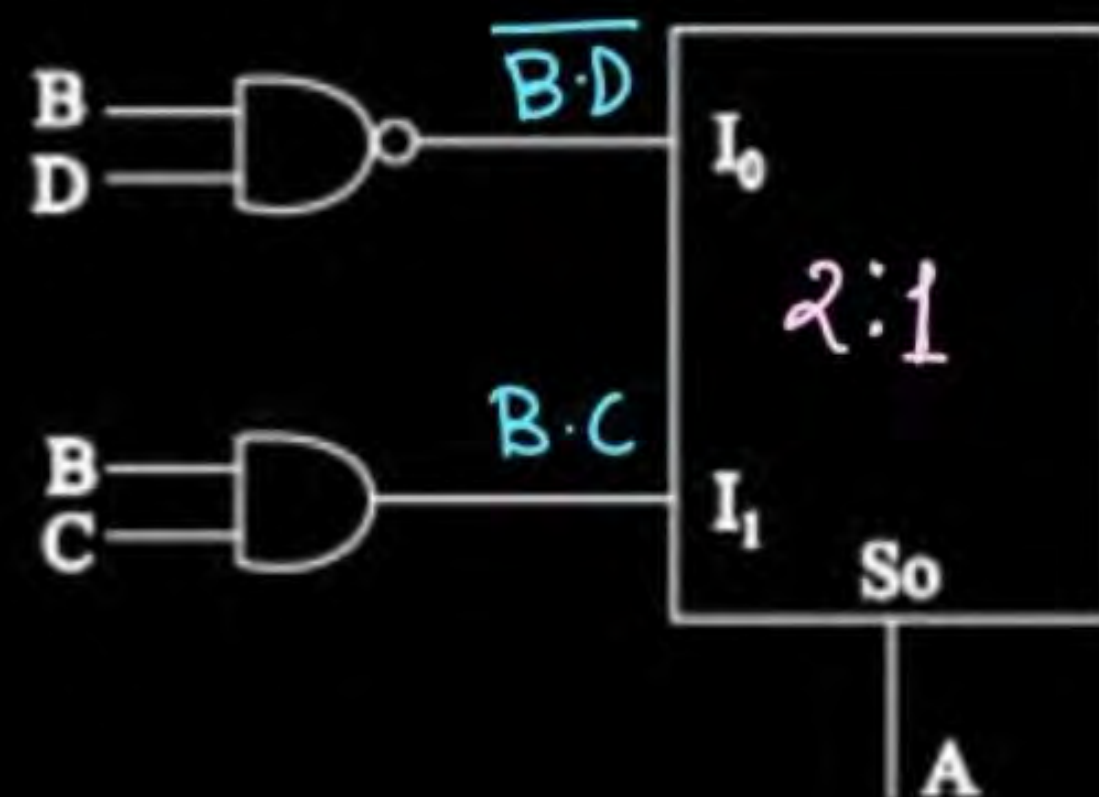

$$\begin{aligned}
 f(A, B, C, D) &= \bar{A} \overline{B \cdot D} + A \cdot BC \\
 &= \bar{A} (\bar{B} + \bar{D}) + ABC \\
 &= \bar{A} \bar{B} + \bar{A} \bar{D} + ABC
 \end{aligned}$$

$f(A, B, C, D)$ is:

A $\Sigma(0, 1, 2, 3, 4, 5, 6, 14, 15)$

B $\Sigma(0, 1, 2, 3, 4, 6, 13, 15)$

C $\Sigma(0, 1, 2, 3, 4, 6, 14, 15)$

D $\Sigma(1, 2, 3, 4, 5, 6, 7, 13, 14, 15)$

$\overline{A}\overline{B}$

0	0	0	0	→	0
0	0	0	1	→	1
0	0	1	0	→	2
0	0	1	1	→	3

 $\overline{A}\quad\overline{D}$

0	0	0	0	→	0
0	0	1	0	→	2
0	1	0	0	→	4
0	1	1	0	→	6

 $\Sigma(0,1,2,3,4,6,14,15)$
 $A\ B\ C$

1	1	1	0	→	14
1	1	1	1	→	15

A MUX ckt is as given below
o/p y is



$$\begin{aligned} y &= A \odot S_0 \\ &= A \odot A \\ &= 1 \end{aligned}$$

$$\begin{aligned} &= \bar{S}_0 \cdot \bar{A} \\ &\quad + S_0 \cdot A \\ &= \bar{A} \cdot \bar{A} + A \cdot A \\ &= A + \bar{A} = 1 \end{aligned}$$

A $\bar{A}$

B A

C 0

D 1

A 4:1 MUX is given as:

D $\bar{x}$ C
 $\bar{D}$ x $\bar{C}$
 $\bar{D}$ x $\bar{C}$
 D $\bar{x}$ C



$$y = 1 \oplus B = \bar{B}$$

$$\begin{aligned}
 y &= C \oplus S_1 \oplus S_0 = A \oplus \bar{A} \oplus B \\
 &= \bar{S}_1 \bar{S}_0 \cdot C + \bar{S}_1 S_0 \cdot \bar{C} + S_1 \bar{S}_0 \bar{C} \\
 &\quad + S_1 S_0 \cdot C
 \end{aligned}$$

$$\begin{aligned}
 f(S_1, S_0, C) &= \sum(1, 2, 4, 7) \\
 &= S_1 \oplus S_0 \oplus C
 \end{aligned}$$

$\bar{x} = D$
 $x = \bar{D}$
 o/p y is

$$\begin{aligned}
 &= D \oplus S_1 \oplus S_0 \\
 &= \bar{x} \oplus S_1 \oplus S_0
 \end{aligned}$$

$$= \bar{x} \oplus S_1 \oplus S_0$$

A $\bar{B}$

B B

C $A \oplus B$


D $A \odot B$

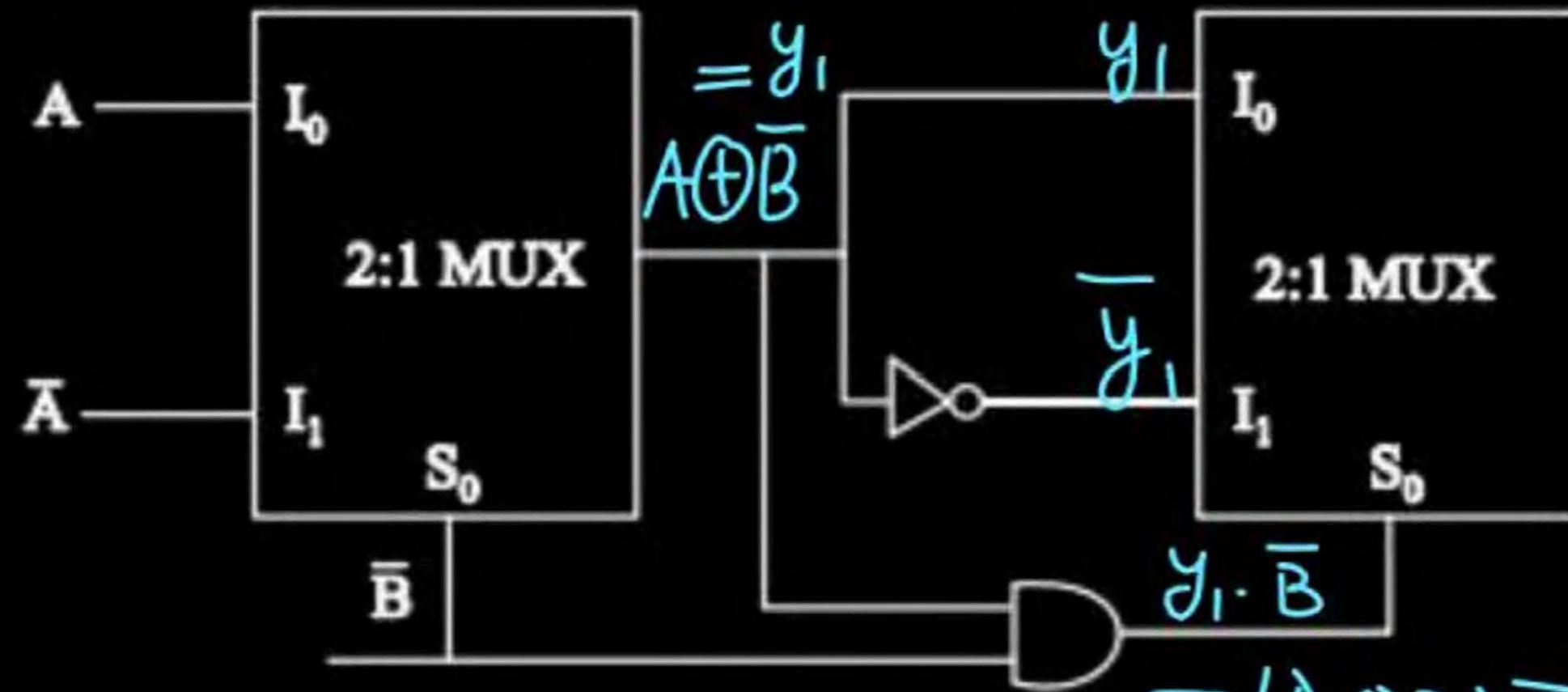Question

MCQ



A combinational ckt is designed using MUX as shown below :-



o/p y is

A $\overline{A+B}$

C $A \oplus B$

B $A \cdot B$

D $A \odot B$

$$A \oplus B \oplus A \cdot B = (A + B)$$

$$A \oplus B \oplus (A + B) = A \cdot B$$

$$y = y_1 \oplus S_0 = A \oplus \bar{B} \oplus (\bar{A} + B)$$


$$= A \oplus B \odot (\bar{A} + B)$$

$$= A \oplus B \oplus (\bar{A} + B)$$

$$= A \cdot B$$

$$= (A \odot B) \bar{B} = (AB + \bar{A}\bar{B})\bar{B} = \bar{A}\bar{B} = \overline{A+B}$$

A MUX circuit is implemented as shown:

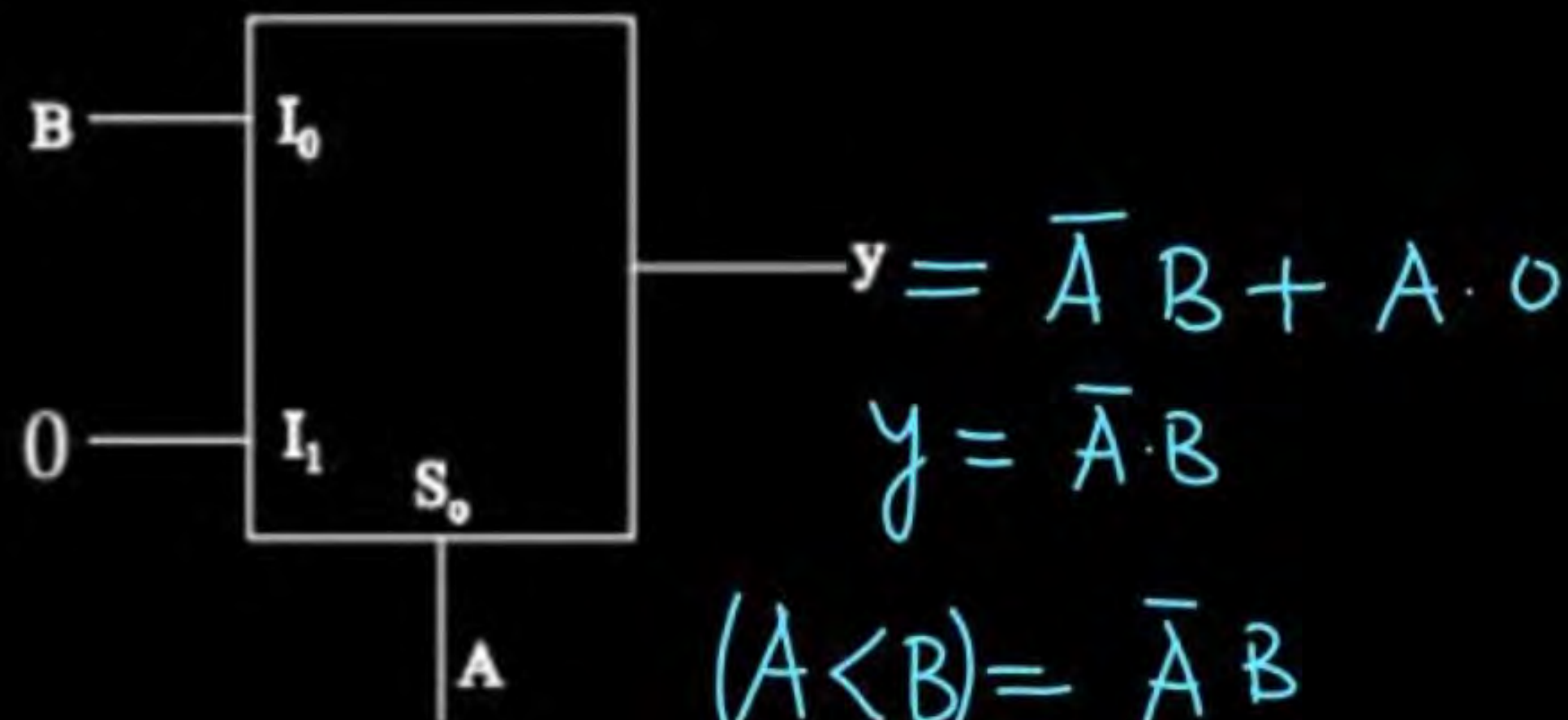

$$(A < B) = \bar{A}B$$

$$(A > B) = A \cdot \bar{B}$$

$$(A = B) = A \odot B$$


A Comparator o/p when $B < A$

B Comparator o/p when $B = A$

C Comparator o/p when $B > A$

D Comparator o/p when $B < 2A$

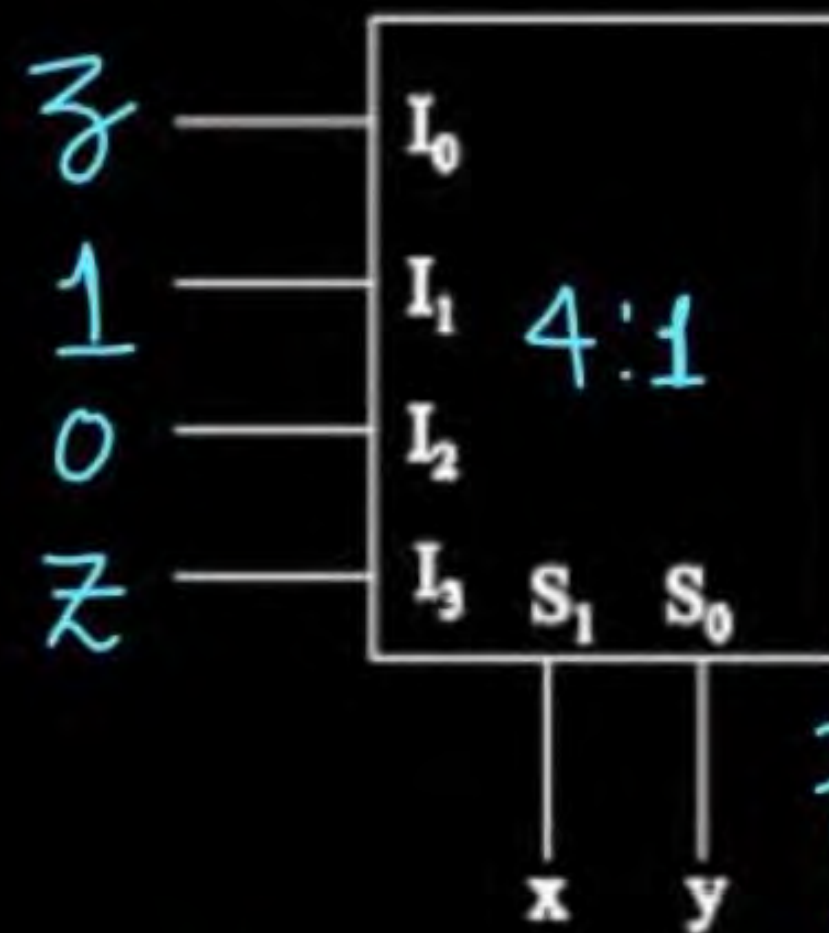In a full subtractor corresponding i/p bits of two no.s are x & y [$x - y$] and input borrow is z and output borrow is B . Output borrow is implemented as shown :



$$B = \bar{x}y + \bar{x}z + yz$$

$$B(x=0, y=0) = \bar{z} + 0 = \bar{z}$$

$$y = \bar{x}y + \bar{x}z + yz$$

$$B(x=0, y=1)$$

$$= 1 + \text{---} = 1$$

Then values of I_0, I_1, I_2 & I_3 are :

☒ **A** $I_0 = z, I_1 = 1, I_2 = 0, I_3 = \bar{z}$

☒ **B** $I_0 = z, I_1 = 0, I_2 = 1, I_3 = \bar{z}$

☒ **C** $I_0 = 1, I_1 = z, I_2 = 0, I_3 = \bar{z}$

☒ **D** $I_0 = \bar{z}, I_1 = 1, I_2 = 0, I_3 = z$

To implement 1024 : 1 MUX, how many 4 : 1 MUXs are required 341.

$$\begin{aligned} N &= \frac{1024}{4} + \frac{256}{4} + \frac{64}{4} + \frac{16}{4} + 1 \\ &= 256 + 64 + 16 + 4 + 1 \\ &= 341 \end{aligned}$$

Which of the following is true:

- A** MUX is non-universal ckt. ✗
- B** ✓ MUX can be used to implement half adder as well as full adder.
- C** ✗ 2:1 MUX has 1-i/p line, 1-o/p line and 2-select lines.
- D** If in a MUX input lines are 24 then minimum 4-select lines are required for proper functioning.

$$M \geq \log_2 N$$

$$M \geq \log_2 24$$

$$M \geq 4.58$$

$$M \geq 5$$




Which of the following is true ?

- A** Decoder and MUX has same internal circuitry ✕
- B** MUX & De MUX has same internal circuitry ✕
- C** ✓ De MUX and decoder has same internal circuitry
- D** None of these



A combinational ckt using decoder and OR gate is as given below :

o/p y_1 & y_2 combinedly represents :

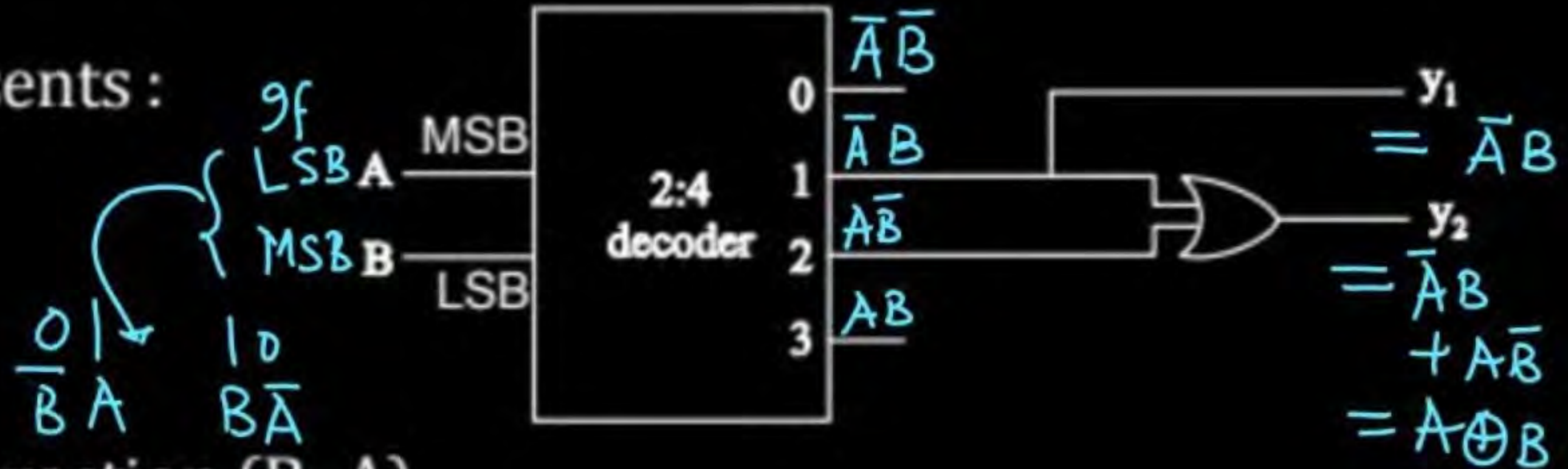

- ☐ **A** Half adder
- ☐ **B** Half subtractor with subtraction ($B-A$)
- ☒ **C** Half subtractor with subtraction ($A-B$)
- ☐ **D** Comparator o/p with ($A > B$)



To implement 1:512 De MUX, we require N, 1:8 De MUX, then the value of N is 73.

$$N = \frac{512}{8} + \frac{64}{8} + \frac{8}{8}$$

$$N = 64 + 8 + 1$$

$$N = 73$$

$$1:128 = (1:2^7) \xrightarrow{1:2} (2^7 - 1) = 127$$

To implement 1:128 De MUX, we require

$$1:128 \xrightarrow{1:4} \underbrace{32 + 8 + 2}_{\downarrow}$$

$$42(1:4)$$

$$+ 1(1:2)$$

$$1:128 \xrightarrow{1:8} \underbrace{16 + 2}_{\downarrow}$$

$$18(1:8) + 1(1:2)$$

A 127 - 1:4 DeMUX ✗

B ✓ 127 - 1:2 DeMUX

C ✓ 18 - 1:8 DeMUX & 1 - 1:2 DeMUX

D ✗ 40 - 1:8 DeMUX & 1 - 1:2 DeMUX



A combinational ckt is as given below

When i/p is $A = 0$ & $B = 1$, then LED no. that glows will be 2.



For a decoder having 4 i/p lines, no. of o/p lines are

A 1


B 2

C 16

D 4

$$n: 2^n$$

A digital ckt is as given below:

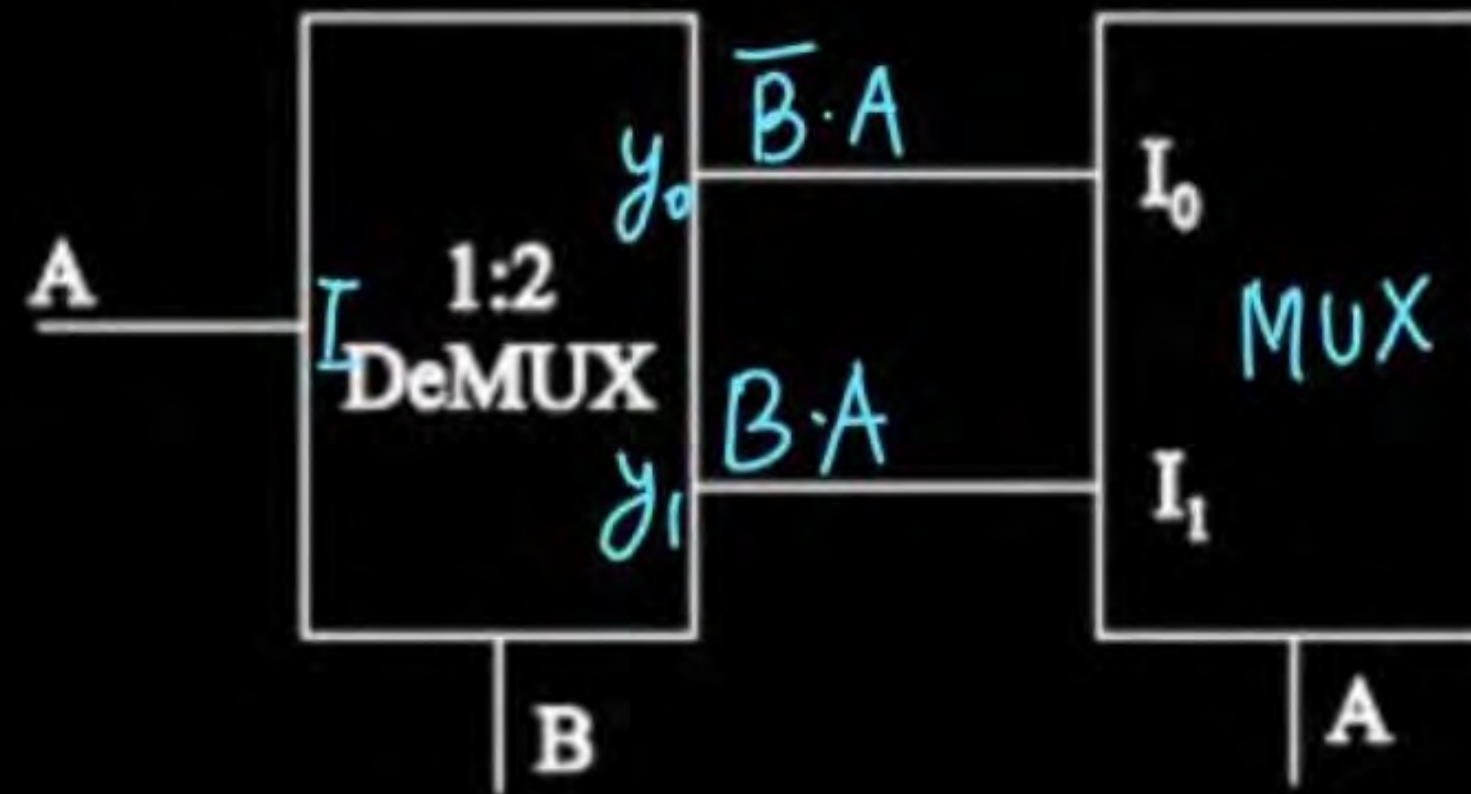

o/p y is

- ☐ A A
- ☒ C A.B

- ☐ B B
- ☐ D $(A + B)$

Which of the following is not true?

A DeMUX is not a universal ckt *→ true*


$$M \geq \log_2 N$$

$$M \geq \log_2 52 \rightarrow M \geq 5.7$$

B For 52 output lines, no. of select lines must be atleast 6 for DeMUX. — *true*


C ✓ DeMUX is parallel to serial converter. *not true*

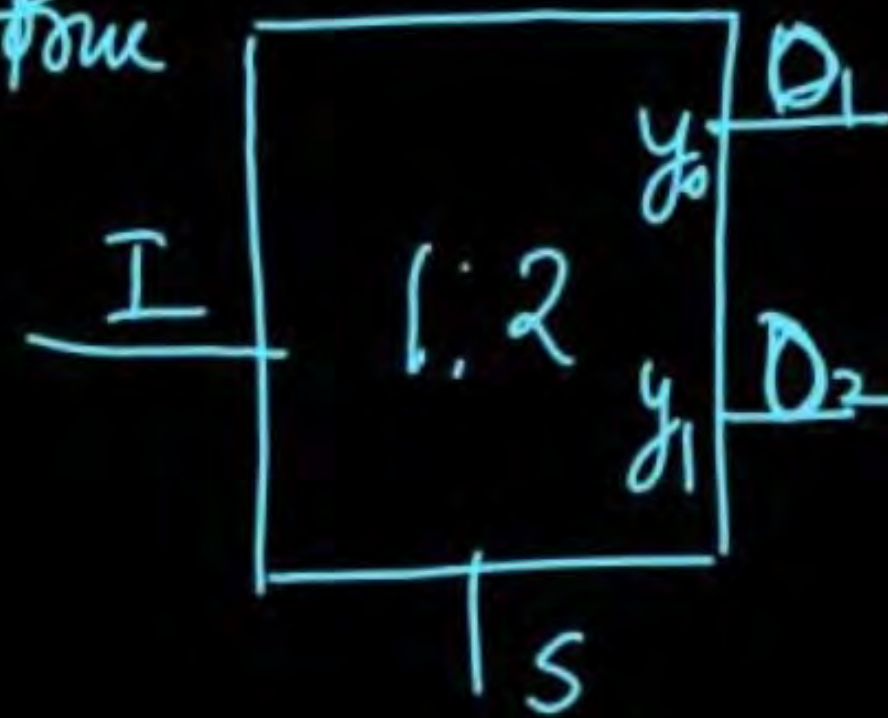D DeMUX is serial to parallel converter *true*




A ckt is as shown below:

o/p y is

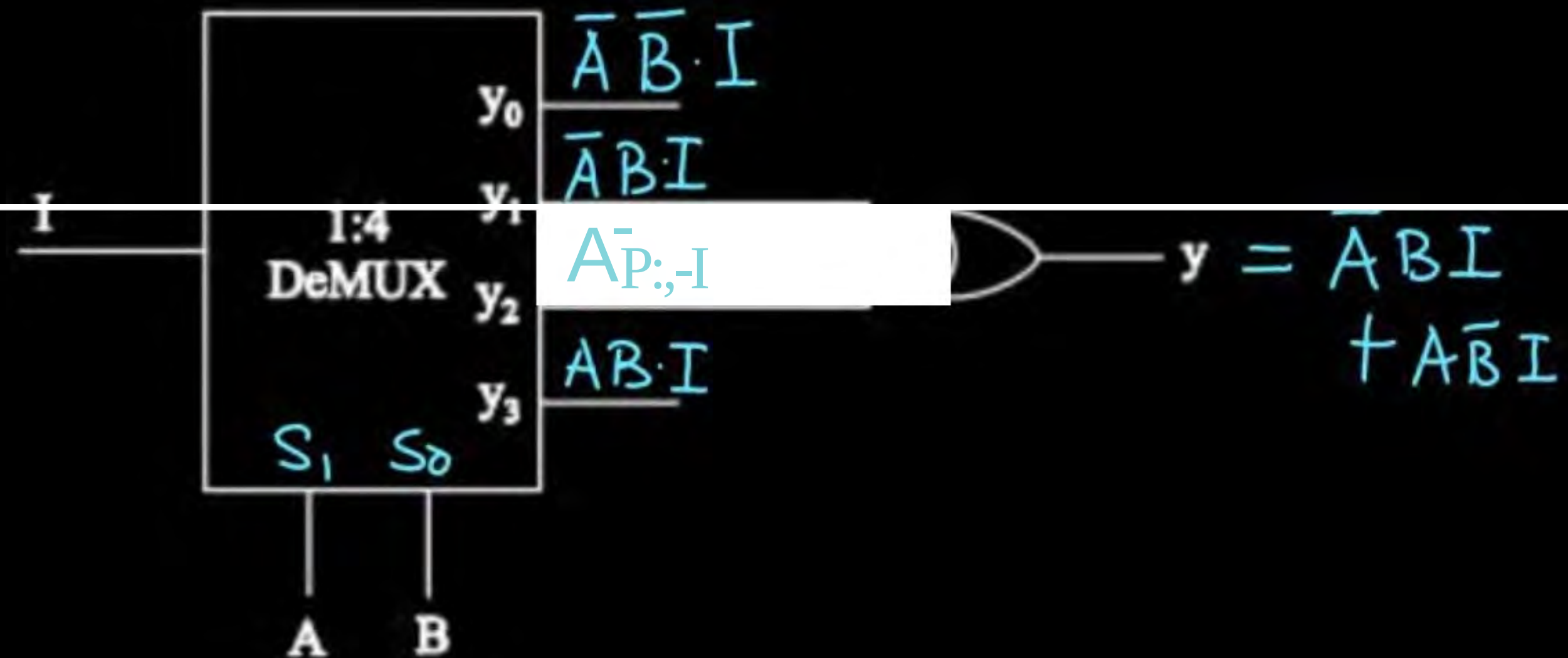

- ☒ **A** $A \oplus B$ if $I = 1$
- ☐ **B** $A \odot B$ if $I = 0$ ✗
- ☐ **C** $A.B$ if $I = 1$ ✗
- ☐ **D** $A + B$ if $I = 0$ ✗

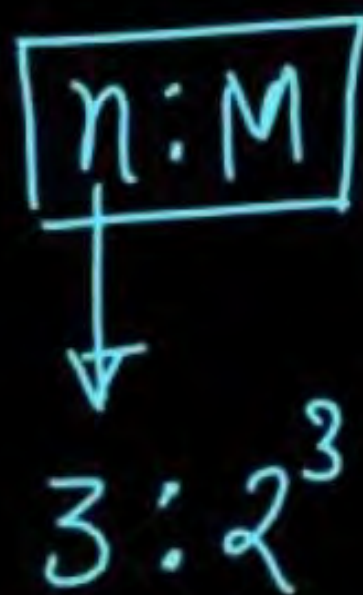For implementing full adder and full subtractor we require a decoder of the order $n:M$, where n is no. of i/p lines & M is no. of o/p lines, then value of M is 8.



$$\text{F.A} \begin{cases} S = f(x, y, z) = \sum(1, 2, 4, 7) \\ C = f(x, y, z) = \sum(3, 5, 6, 7) \end{cases}$$

$$\text{F.S} \begin{cases} D = f(x, y, z) = \sum(1, 2, 4, 7) \\ B = f(x, y, z) = \end{cases}$$

Question MSQ (C)

no. of i/p lines = 4

4-i/p lines XNOR $\rightarrow$

It is given that:

$x_1 \odot x_2 \odot x_3 \odot x_4 = 0 \rightarrow$ at i/p side odd no. of 1's are there. $\rightarrow$ one 1's or three 1's

Then which of the following is/are true?

A $x_1 x_2 + x_3 x_4 = 1$ $\times$

B $x_1 \oplus x_2 + x_2 \oplus x_3 + x_3 \oplus x_4 = 1$ $\times$

C Sum of x_1, x_2, x_3 & x_4 will be odd. $\checkmark$

D $\overline{x_1 x_2} + x_2 x_3 + \overline{x_3 x_4} = 1$ $\times$


1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

1	0	1	0
---	---	---	---

one i/p line is at '1' & other three are at '0'

A digital circuit is as given below:

Output y is

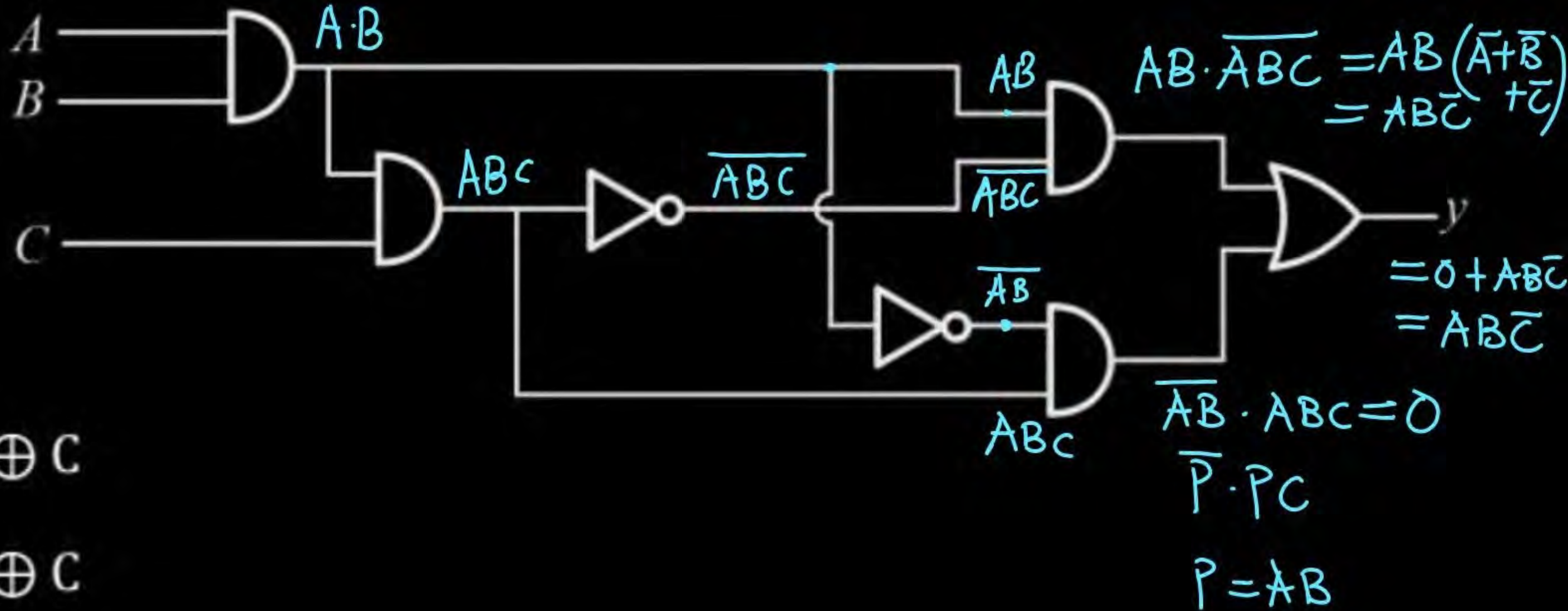

A ABC

B $A \oplus B \oplus C$

C $A \odot B \oplus C$

D $\overline{A+B+C}$



$$P = \overline{\text{Carry}} = \overline{xy + yz + zx} \quad \text{Carry} = \sum(3, 5, 6, 7)$$

A circuit is designed as shown: $= (\overline{x+y})(\overline{y+z})(\overline{z+x})$ $P = \sum(0, 1, 2, 4)$

Output P is 1 when majority of input lines are '0'.

Output P is


$$= \overline{x} \overline{y} + \overline{y} \overline{z} + \overline{z} \overline{x}$$

A $xy + yz + zx$ ✗

B $\overline{x} \overline{y} + \overline{y} \overline{z} + \overline{z} \overline{x}$ ✓

C $\overline{x+y+z}$ ✗

D $\overline{xy + yz}$ ✗

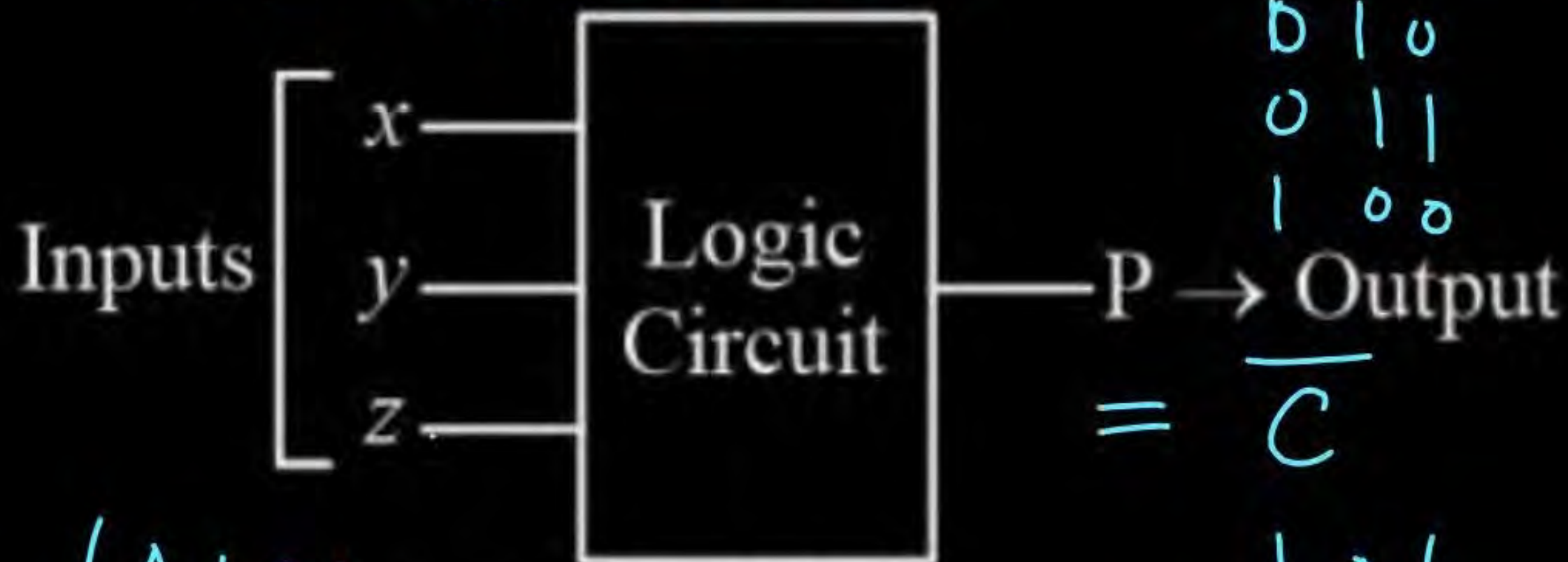

$$= \overline{C}$$

$$(A+B)(B+C)(C+A)$$

$$AB + BC + CA = (A+B)(B+C)(C+A)$$

		Carry	P
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0




Two logical functions:

$$f_1(A, B) = \Sigma(1, 2)$$

$$f_2(A, B) = \Sigma(0, 1, 3)$$

then output $f(A, B)$ will be

$$\bar{f}_2(A, B) = \Sigma(2)$$

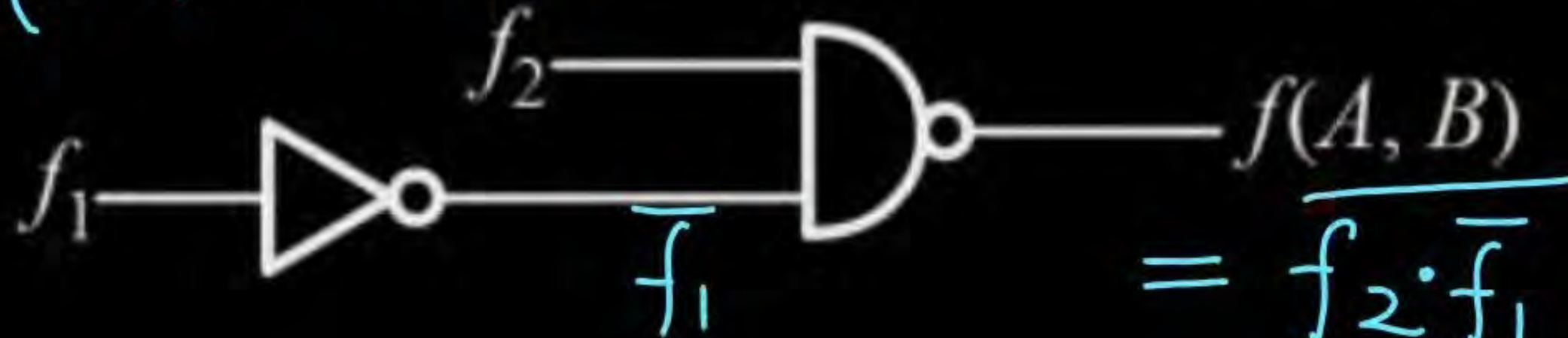

$$= \overline{f_2 \cdot \bar{f}_1}$$

$$= \bar{f}_2 + f_1$$

$$= \Sigma(1, 2)$$

☒ **A** $\Sigma(1, 2)$

☐ **B** $\Sigma(0, 1, 3)$

☐ **C** $\Sigma(0, 1, 2, 3)$

☐ **D** $\Sigma(1)$

A K-Map is as given below:
Its simplified solution will be

A $(\bar{A} + \bar{B})\bar{C}$

B $(\bar{A} + \bar{B})(\bar{A} + \bar{C})$

C $\overline{AB} + \overline{BC}$



D None of these

$$f$$

	$\bar{B}$	B
$\bar{A}$	X	1
A	$\bar{C}$	


$$= (\bar{A} + \bar{B})\bar{C}$$
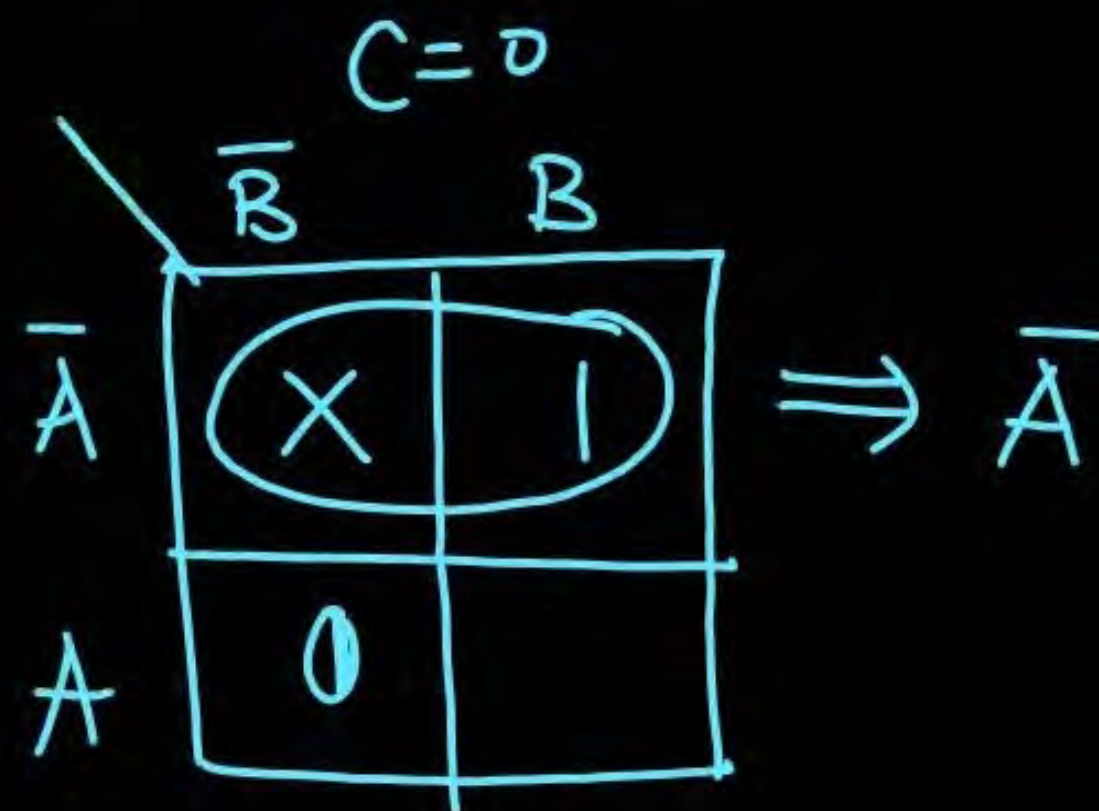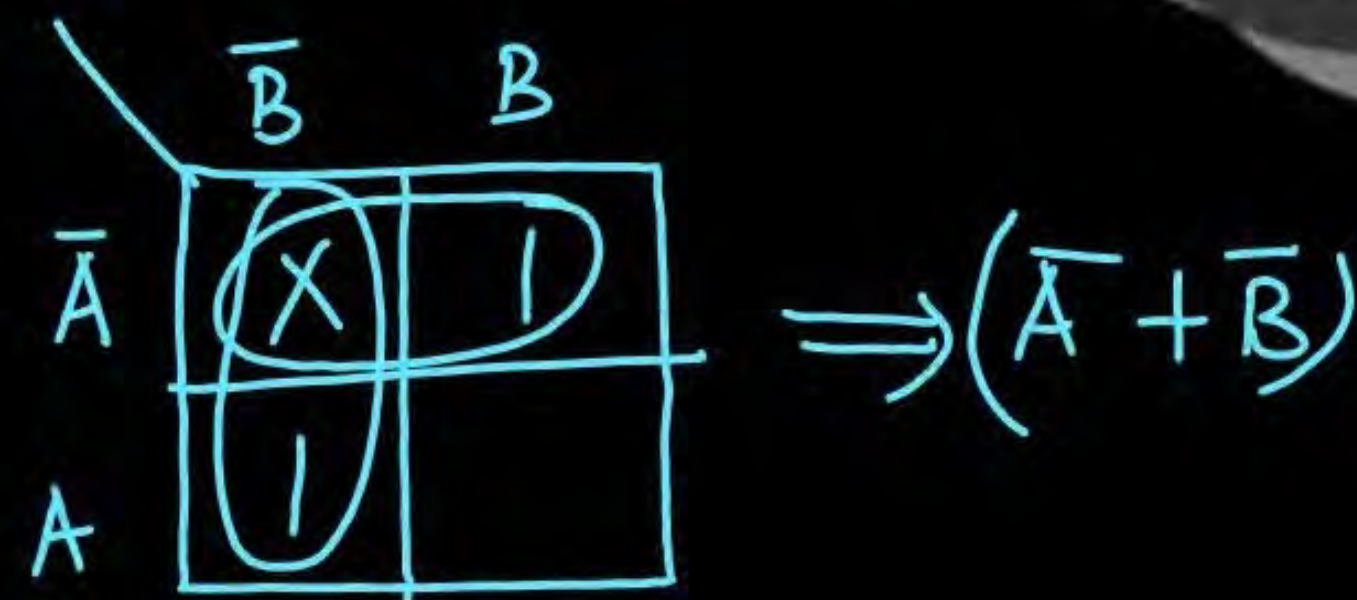
$$= \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{A}C = \bar{A}(\bar{C} + C) + \bar{B}\bar{C} = \bar{A} + \bar{B}\bar{C} = (\bar{A} + \bar{B})(\bar{A} + \bar{C})$$



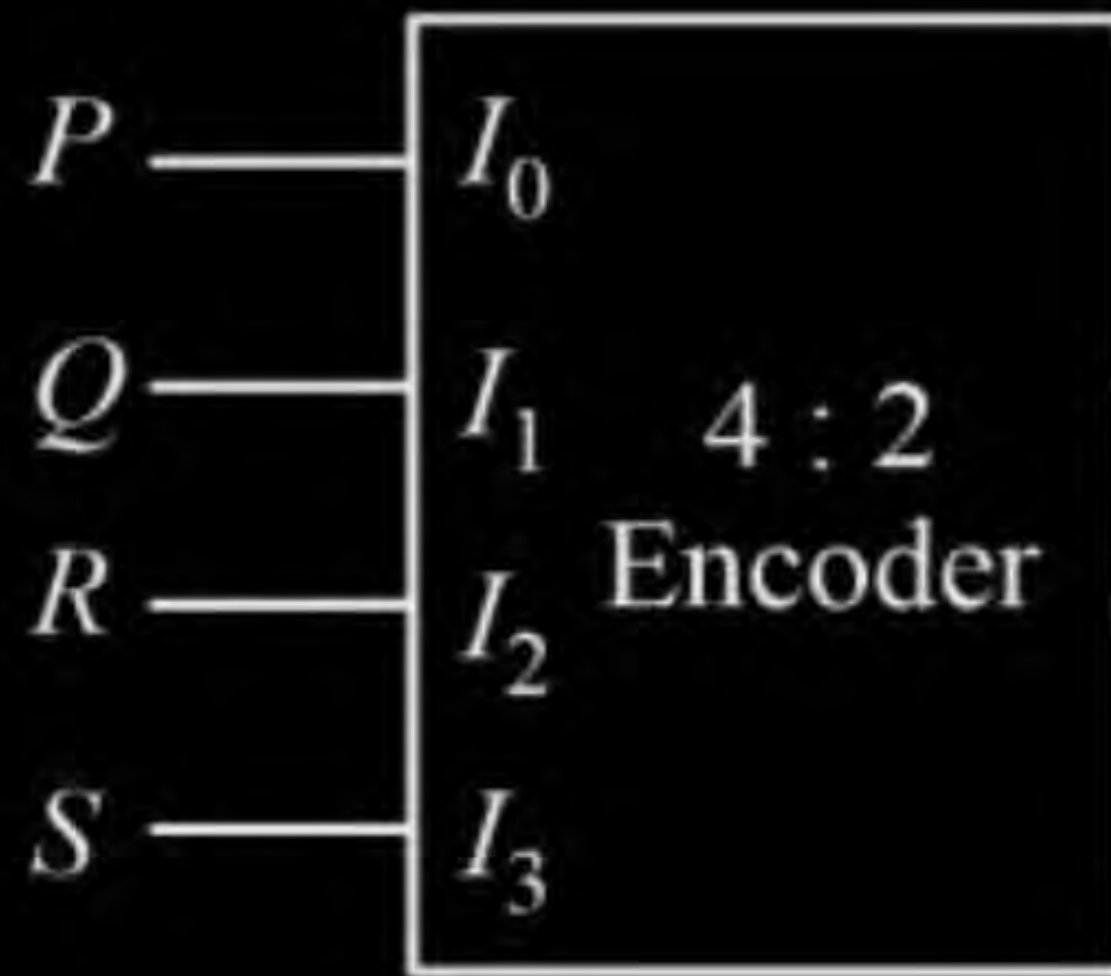Question**MCQ**

A 4 : 2 Encoder is as given below:
Output y_1 will be



I_0	I_1	I_2	I_3	y_1	y_0
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

$$y_1 = I_2 + I_3 = (R + S)$$

$$y_0 = I_1 + I_3 = (Q + S)$$

- A** $(P + Q)$
- B** $(Q + R)$
- C** $(R + S)$
- D** $(P + S)$

Which of the following is not true?

☒ A

$$A + \bar{B}C = (A + \bar{B})(\bar{B} + C) \xRightarrow{\text{not true}} A + (\bar{B} \cdot C) = (A + \bar{B}) \cdot (A + C)$$

☐ B

$$\bar{A} + \bar{B}C = \overline{AB} \cdot (\bar{A} + C) \xrightarrow{\text{true}} \bar{A} + (\bar{B} \cdot C) = (\bar{A} + \bar{B}) \cdot (\bar{A} + C) = \overline{A \cdot B} (\bar{A} + C)$$

☐ C

$$AB + \bar{A}C + \bar{B}C = AB + \bar{B}C \quad \text{true} \quad \text{f } AB + BC = (A+B)(B+C) \quad \text{not true}$$

☐ D

$$AB + BC + AC = (A+B)(B+C)(C+A) \quad \text{true} \quad \text{f } \downarrow = (A+B) \cdot (B+C)$$

For n -variable, the number of self dual functions are found to be 256, then the value of n is 4.

$$\text{no. of boolean functions} = 2^{2^n} = 2^{2^4} = 2^{16} = 256 \times 256$$

$$\text{no. of self dual functions} = 2^{2^{n-1}} = 256 = 2^8$$


$$2^{n-1} = 8 = 2^3$$

$$n-1 = 3$$

$$n = 4$$

To add two 5 bit numbers, we required m H.A.s and n-OR gates then minimum value of $(m+n)$ 13. $N \rightarrow$ bit number $\Rightarrow$

9 HA
4 OR

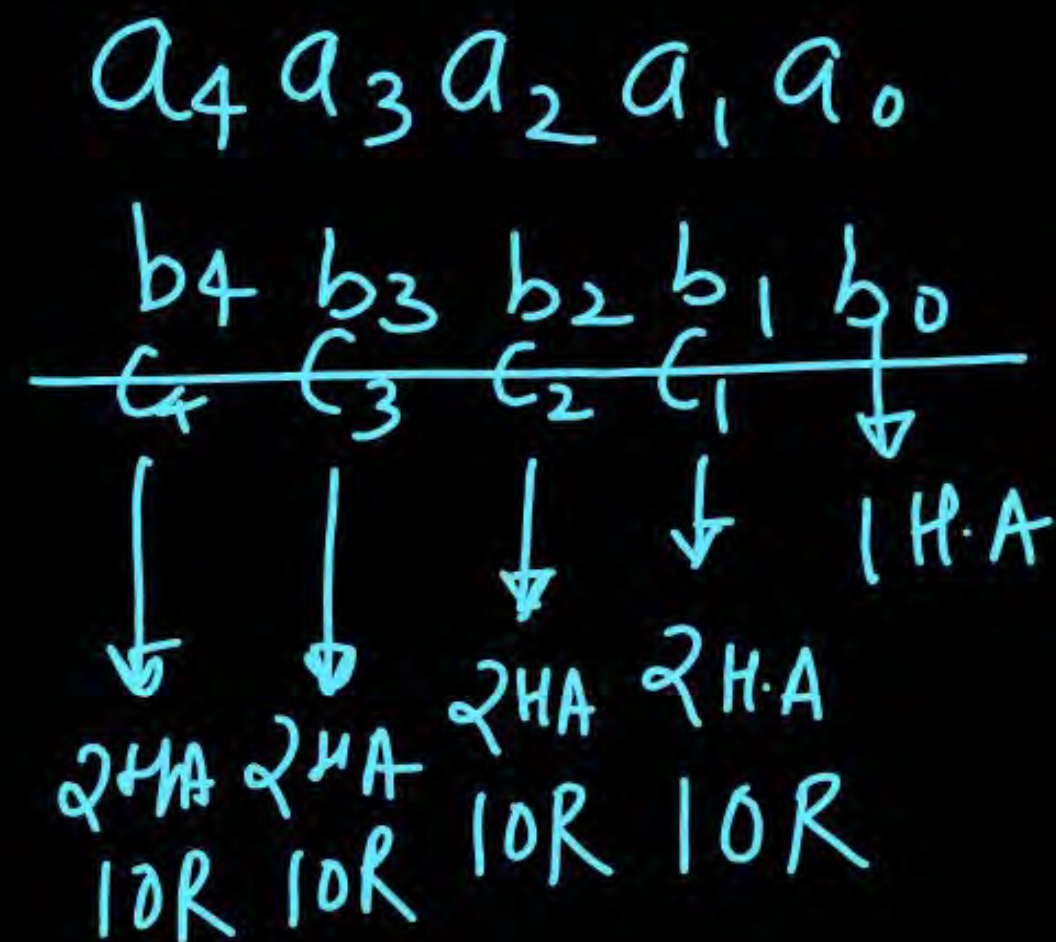

Two stage SOP circuit can directly be implemented

- ☒ **A** ~~X~~ Using NAND gates at first stage & AND gate at second stage. ~~X~~
- ☒ **B** ✓ Using NAND gates only at both first & second stage.
- ☒ **C** ~~X~~ Using NOR gates only at both first & second stage.
- ☐ **D** None of these

Thank you

GW
Soldiers!

